



Queen Mary

University of London

Science and Engineering

## **EBU4202: Digital Circuit Design Tutorials (Block 4)**

Dr. Md Hasanuzzaman Sagor (Hasan)

Dr. Chao Shu (Chao)

Dr. Farha Lakhani (Farha)

School of Electronic Engineering and Computer Science,  
Queen Mary University of London,  
London, United Kingdom.

# Question 1&2

---

1. Explain what is meant by each of the following terms:

- Non-volatile
- Random Access
- DRAM
- EPROM

2. Using a suitable diagram, briefly explain the function of a DECODER.

# Question 3

---

- Suppose we have a computer with 256 MBytes of memory, with each memory chip having a capacity of 4 MBytes.
  - i) How many memory chips are required?
  - ii) How many address bits are required?
  - iii) How many bits are required to select the memory chips?
  - iv) Draw a block diagram of a circuit using a decoder so that all 256 Mbytes of memory can be addressed.

# Question 4

Design a 16 x 1-bit read-only memory (ROM) circuit pre-programmed with the data shown in the following table.

Address	Data
0	0
1	1
2	0
3	0
4	1
5	1
6	1
7	1
8	1
9	0
10	0
11	1
12	0
13	0
14	1
15	1

# Question 5

Design an 8 x 4-bit read-only memory (ROM) circuit pre-programmed with the data shown in the Table below. (Hint: diodes, decoder, multiplexer etc. are required in this ROM design).

Address	Data (4 bit)
0	4
1	9
2	10
3	12
4	15
5	1
6	3
7	0

# Question 6

---

Draw the Block Diagram of a Microcomputer showing CPU, memory and the three busses.

# Question 7

Design an 8 x 4-bit read-only memory (ROM) circuit pre-programmed with the data shown in the Table below. (Hint: diodes, decoder, multiplexer etc. are required in the ROM circuit).

Address	Data (4 bit)
0	8
1	15
2	8
3	0
4	14
5	14
6	1
7	1