

---

Beijing University of Posts and Telecommunications  
No.10 Xitucheng Road,  
Haidian District,  
Beijing, China  
010-67374537

June 2,2015  
Yang Qixuan  
[2013213059@bupt.edu.cn](mailto:2013213059@bupt.edu.cn)

## Transistor amplifying circuit

### Experiment equipment


1. Digital multi-tester
2. DC stabilized voltage power supply.
3. Function signal generating device
4. AC millivolt
5. Double-trace oscilloscope

### Preparation requirements

1. Transistor amplifying circuit's principle of working.
2. Amplifying circuit static state working point measuring and debugging
3. Research amplifying circuit's dynamic working principle.

### Experience content

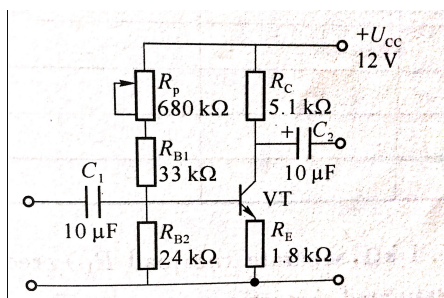
1. The measurement of the amplifying circuit static state working point.
  - (1) Judge triode's polarity and the quality with the multi-tester.
  - (2) According to Figure junction circuit, connect direct -current power supply, measure  $V_B$ ,  $V_E$ ,  $V_C$ ,  $R_P$ , with the multi-tester, and calculate  $U_{CE}$ ,  $I_B$ ,  $I_C$  and fill in table 9.1



Measured value				Calculate value		
$V_B$	$V_E$	$V_C$	$R_P$	$U_{CE} (V)$	$I_B (mA)$	$I_C (mA)$
2.0596	1.4430	7.828	7.545	5.7684	0.0163	0.8180

## 2. Dynamic research

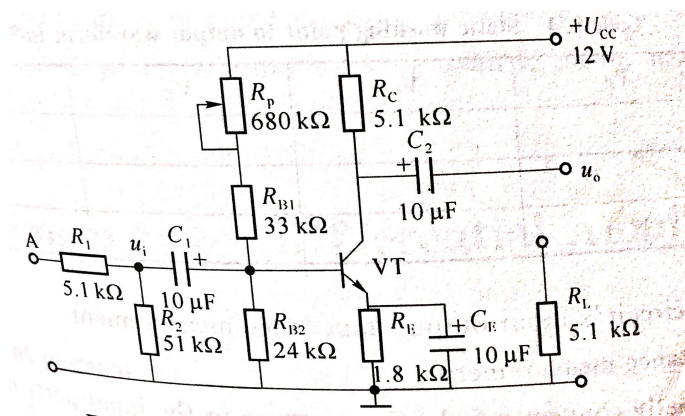- (1) According to Figure junction circuit, adjusts  $R_P$  to cause  $V_C$  to be equal to 6V
- (2) Adjust signal generator's output for the sinusoidal signal of  $f=1KHZ$   $U_S = 500mV$  and connect to table electric circuit's A spot, through  $R_1$ ,  $R_2$  attenuation 100 times, the signal which the  $u_i$  obtain 5mV, and observe  $u_i$ ,  $u_o$  signal, pay attention to phase relation, and draw  $u_i$ ,  $u_o$  waveform.
- (3) Maintain the signal generating device output signal frequency invariable, increase the signal scope gradually, observe the most greatly not distorted voltage  $u_o$  and fill in table.



Measuring		Calculating	Estimating
$u_i$ (mV)	$u_o (V)$	Au	Au
6.20	-0.890	-143.5	-170.4
8.20	-1.290	-157.3	-183.2

10.1	-1.590	-157.4	-185.2
------	--------	--------	--------

(4) Maintain  $u_i = 5\text{mV}$  to be invariable, when idling tune  $V_C = 6\text{V}$ , and the load is connected to the amplifying circuit, according to parameter condition table, which assign measurement, and the computed result will fill in the table.

Assigns the parameter		Measuring		Calculating	Estimating
$R_C (\text{K}\Omega)$	$R_L (\text{K}\Omega)$	$u_i (\text{mV})$	$u_o (\text{mV})$	Au	Au
5.1	5.1	5	-388	-77.6	-87.66
5.1	2.2	5	-236	-47.2	-58.82
2	5.1	5	-218	-43.6	-52.27
2	2.2	5	-152	-30.4	-40.45

(5)  $u_i = 5\text{mV}$  reduced  $R_P$ , cause  $V_C < 4\text{V}$  may observe the saturated distortion, increase  $R_P$ , cause  $V_C > 9\text{V}$  may observe the saturated distortion may observe to cut off distorts, the measurement result will fill in table.

$R_P$	$V_B$	$V_C$	$V_E$	Output waveform situation
Small	3.84	3.20	3.18	Saturated distortion
Appropriate	2.76	5.90	2.13	Normal
Big	1.361	11.055	1.06	Cut off distorts

## Conclusion

1. Grasp the measuring method of the amplifying circuit static state working point and analyze the influence of the static state working point to the amplifier performance.
2. Grasp the measuring method of the amplifying circuit voltage amplification gain and the most greatly not distorted voltage.
3. Grasp the measuring method of the amplifying circuit input resistance and output impedance.

I will call you this week to discuss our study and any possible follow-up you wish us to do.

Sincerely,  
Yang Qixuan