



Queen Mary

University of London

Science and Engineering

## **EBU4202: Digital Circuit Design**

### **Hazards and Glitches**

Dr. Md Hasanuzzaman Sagor (Hasan)

Dr. Chao Shu (Chao)

Dr. Farha Lakhani (Farha)


School of Electronic Engineering and Computer Science,  
Queen Mary University of London,  
London, United Kingdom.

# Timing Hazards and Output Glitches

- *Output glitch*: A momentary unexpected output change (short pulse) when an input changes; usually caused by gate propagation delays.
- *Hazards*: A timing hazard exists in a combinational circuit when it produces an *output glitch* when one or more inputs change.
  - Static Hazards (*static-1* and *static-0*): when 1 input variable changes, the output changes momentarily before stabilising on the correct value.
    - Can usually be fixed by adding redundant logic
  - Dynamic Hazards: possibility of an output changing more than once as a result of a single input change.


# Timing Hazards and Output Glitches

- Example of *static-1 hazard*

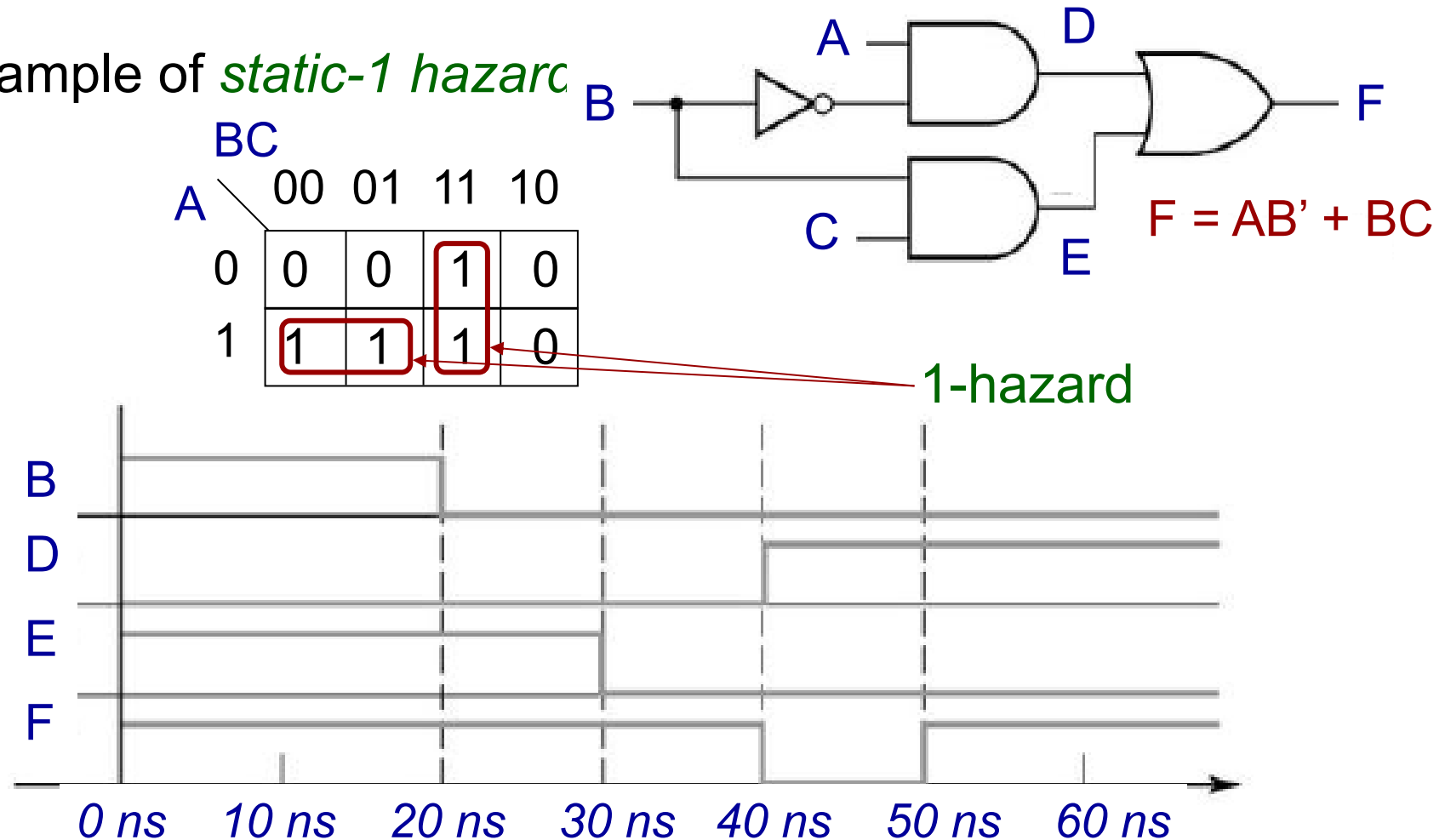

# Timing Hazards and Output Glitches


- Example of *static-1 hazard (cont.)*:

 

|   |   | BC |    |    |    |
|---|---|----|----|----|----|
| A |   | 00 | 01 | 11 | 10 |
|   | 0 | 0  | 0  | 1  | 0  |
|   | 1 | 1  | 1  | 1  | 0  |

removing the  
*static-1 hazard*

$$F = AB' + BC + AC$$

 

# Static Hazards

- A **static-1 hazard** is a pair of input combinations that: (i) differ in only one input variable and (ii) both give a 1 output; such that it is possible for a momentary 0 output to occur during a transition in the differing input variable.
- A **static-0 hazard** is a pair of input combinations that: (i) differ in only one input variable and (ii) both give a 0 output; such that it is possible for a momentary 1 output to occur during a transition in the differing input variable.


# Timing Hazards

**Question:** Is there any static hazard on the combinational circuit shown in the Karnaugh Maps? How can we eliminate this?

|   |   | BC |    |    |    |
|---|---|----|----|----|----|
|   |   | 00 | 01 | 11 | 10 |
| A | 0 | 0  | 0  | 1  | 1  |
|   | 1 | 0  | 1  | 1  | 0  |

# Timing Hazards

$$F = A' \cdot B + A \cdot C$$

 

| A | BC |    |    |    |
|---|----|----|----|----|
|   | 00 | 01 | 11 | 10 |
| 0 | 0  | 0  | 1  | 1  |
| 1 | 0  | 1  | 1  | 0  |

F

STATIC - 1 HAZARD ('RACE' HAZARD)

IF ONE OF THE AND GATE OUTPUTS  
GOES TO 0 BEFORE THE OTHER.

# Timing Hazards

Is there any static hazard on the combinational circuit shown in the Karnaugh Maps? How can we eliminate this?


**Answer:** add a redundant group:

|   |   | BC |    |    |    |
|---|---|----|----|----|----|
|   |   | 00 | 01 | 11 | 10 |
| A | 0 | 0  | 0  | 1  | 1  |
|   | 1 | 0  | 1  | 1  | 0  |



# Timing Hazards

$$F = A'.B + A.C + B.C$$

 

STATIC - 1 HAZARD ELIMINATED

|   |   | BC |    |    |    |
|---|---|----|----|----|----|
|   |   | 00 | 01 | 11 | 10 |
| A | 0 | 0  | 0  | 1  | 1  |
|   | 1 | 0  | 1  | 1  | 0  |
|   |   | F  |    |    |    |

# Timing Hazards

*Example:  $F = X'Y'Z + X'YZ' + XYZ = (X \oplus Y)' \cdot Z + (X + Z)' \cdot Y$*

*Three input combinations give output 1.*

*$XYZ = 001$*

*$XYZ = 010$*

*$XYZ = 111$*

|   |   |    |    |    |    |    |
|---|---|----|----|----|----|----|
|   |   | YZ | 00 | 01 | 11 | 10 |
| x | 0 |    | 0  | 1  | 0  | 1  |
|   | 1 |    | 0  | 0  | 1  | 0  |

*If we investigate any two input combinations, we see that there are two variable changes. So, no Static-1 Hazard.*

*But according to the static-0 definition, there is a possibility to exist a Static-0 hazard (for input combinations  $XYZ = 000, 100$ ).*

*However, a properly designed two-level SoPs (AND-OR) circuit has no Static-0 hazard. You can draw the corresponding timing diagram for both circuits and check if there is any hazard.*

# Timing Hazards

