



Queen Mary

University of London

Science and Engineering

EBU4202: Digital Circuit Design
Basic Logic Functions and Switching Algebra

Dr. Md Hasanuzzaman Sagor (Hasan)

Dr. Chao Shu (Chao)

Dr. Farha Lakhani (Farha)

School of Electronic Engineering and Computer Science,
Queen Mary University of London,
London, United Kingdom.

Overview: Switching Algebra & Combinational Logic Design

- * **Switching Algebra**
- * **Combinational Circuit Analysis & Synthesis**




Chapters 4 & 6 – “Digital Design: Principles and Practices” book

Combinational Logic Circuits: Analysis & Synthesis

- **Digital Circuits:**

 - **Combinational Logic Circuit:** a circuit whose outputs depend on its current inputs.
- **Sequential Logic Circuit:** a circuit whose outputs depend not only on current inputs, but also on past inputs.



- These slides are concerned with the **analysis** and **synthesis** of **combinational** logical **circuits**.

- **Analysis** → start from a logic diagram of a circuit and derive a formal description of the function of the circuit.
- **Synthesis** → start with a formal description of the function of a circuit and proceed to a logic diagram that performs the required function.



Studied later
in the course.


Switching Algebra

- Switching Algebra:

- Two-valued boolean algebra (George Boole 1815-64)

- For a variable X :

- $X=0$ or $X=1$

 

No other values are allowed.

- Many other possible “boolean” representations:


- $X = \text{Light on}$ or $X = \text{Light off}$

- $X = \text{voltage HIGH}$ or $X = \text{voltage LOW}$

- Basic operations are AND, OR and complement (or *invert*) (AND/OR/NOT).

Basic Gates (1/3): AND

 - Performs the **AND logic operation** on its **inputs** and **outputs** its result.




Truth table →

Binary ascending
counting order.

Input		Output
A	B	F
0	0	0
0	1	0
1	0	0
1	1	1


**Circuit
Switching
Diagram** →

 

Switching Algebra Equation → $F = A.B$ or $F = AB$

Basic Gates (2/3): OR

 
- Performs the **OR logic operation** on its *inputs* and *outputs* its result.



Truth table →

Input		Output
A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

Circuit Switching Diagram →

 

Switching Algebra Equation → $F = A + B$

Basic Gates (3/3): NOT



Other notation (not used here): $F = \sim A$ or $F = \neg A$.

- Also called an **inverter**, it produces an **output** value that is the opposite of the **input** value.




Truth table →

Input A	Output F
0	1
1	0

Switching Algebra Equation → $F = A'$ or $F = \bar{A}$

Circuit Switching Diagram →

 


Example: Combining Basic Gates

- Any *Boolean function* can be represented with a Truth Table.

Switching Algebra

$$F(X,Y,Z) = X + \overline{Y}.Z$$

Logic Gate Diagram

 

Truth Table

X	Y	Z	$F = X + \overline{Y}.Z$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

More Gates

- There are **more gates available for the designer** to use than those discussed so far.
- Of particular importance to the electronics industry are the **Buffer**, **NAND**, **NOR**, **Exclusive-OR** and **Exclusive-NOR** gates.
 - **NAND** and **NOR** gates are particularly important because they **are faster than AND** and **OR** gates.



Any digital circuit of any complexity can be made from **NAND** gates.




Why do you think that is the case?.....to answer this you need to look at the circuits that are inside the gates.....

Other Gates (1/5): Buffer

- Also called a **non-inverting buffer**, it asserts its **output** signal if and only if its **input** is asserted.

Symbol →

 


Truth table →

A	F
0	0
1	1

Switching Algebra Equation → $F = A$


Circuit
Switching
Diagram →

 

NOTE: You might ask the question “Why do we need this gate, it does not seem to do anything”. It has important input and output characteristics that make it useful in practical circuits.

Other Gates (2/5): NAND

 - It does the *opposite of* an **AND** gate.



Truth table →

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

Switching Algebra Equation →


$$F = (A.B)' \text{ or}$$

$$F = (AB)' \text{ or}$$

$$F = \overline{(A.B)} \text{ or}$$


$$F = \overline{(AB)}$$

Circuit Switching Diagram →

 

Other Gates (3/5): NOR

- It does the *opposite of* an OR gate.

 


Truth table →

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

Switching Algebra Equation →


$$F = (A+B)'$$
$$F = \overline{(A+B)}$$

Circuit Switching Diagram →

 

Other Gates (4/5): XOR

 - Its *output* is *high*, only when the *inputs are different*.




Truth table →

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

Switching Algebra Equation → $F = (A \oplus B)$ or
 $F = A'B + AB'$ or
 $F = \bar{A}B + A\bar{B}$


XOR=Exclusive OR

Circuit
Switching
Diagram →

 

Other Gates (5/5): XNOR

- It does the *opposite of* an XOR gate.

 

Truth table →

A	B	F
0	0	1
0	1	0
1	0	0
1	1	1

Switching Algebra Equation →

$$F = (A \oplus B)'$$


$$F = \overline{(A \oplus B)}$$

$$F = A'B' + AB$$

$$F = \overline{A}\overline{B} + AB$$

XNOR=Exclusive NOR

Circuit Switching Diagram →

 

Why do we manipulate equations?

- Before we get to the theorems, **why worry about manipulating Boolean equations?**
 - Simplification of digital circuits.
 - Fewer gates required.
 - Potential for faster operation.
 - Smaller is always better!!

Switching Algebra: Basic Definitions

- **Literal**: variable or the complement of a variable.
 - Examples: X, Y, X', Y'
- **Product Term**: single literal or logical product of 2+ literals.
 - Examples: $X, X \cdot Y \cdot Z', X \cdot Y'$
- **Sum of Products Expression (SOP)**: logical sum of product terms
 - Example: $X \cdot Z' + X \cdot Y \cdot Z' + X \cdot Y'$
- **Sum Term**: single literal or logical sum of 2+ literals.
 - Examples: $X, X + Y + Z', X + Y'$
- **Product of Sums Expression (POS)**: logical product of sum terms
 - Example: $(X + Z') \cdot (X + Y + Z') \cdot (X + Y')$

Precedence Rules & Axioms

- **Precedence Rules:** $'$, \cdot and $+$.
- **Axioms:**
 - A minimum set of basic mathematic definitions that are assumed to be always **True** and from which we can derive theorems.
 - Let **X** be a logic variable taking on values **0** or **1**.

$$(A1) \quad X=0 \text{ if } X \neq 1$$

$$(A1') \quad X=1 \text{ if } X \neq 0$$

$$(A2) \quad X=0 \text{ then } X'=1$$

$$(A2') \quad X=1 \text{ then } X'=0$$

$$(A3) \quad 0 \cdot 0 = 0$$

$$(A3') \quad 1 + 1 = 1$$

$$(A4) \quad 1 \cdot 1 = 1$$

$$(A4') \quad 0 + 0 = 0$$

$$(A5) \quad 0 \cdot 1 = 1 \cdot 0 = 0$$

$$(A5') \quad 0 + 1 = 1 + 0 = 1$$

Single Variable Theorems & Perfect Induction

- Let **X** be a logic variable:

(T1) $X+0 = X$	(T1') $X \cdot 1 = X$
(T2) $X+1 = 1$	(T2') $X \cdot 0 = 0$
(T3) $X+X = X$	(T3') $X \cdot X = X$
(T4) $(X')' = X$	
(T5) $X+X' = 1$	(T5') $X \cdot X' = 0$



These theorems can be proved using axioms via *perfect induction*.

- Perfect Induction** (better known as *common sense*).

– *Example*:

- (T1') $X \cdot 1 = X$

2 possible values for literal **X** $\left\{ \begin{array}{l} [X = 0] \rightarrow 0 \cdot 1 = 0 \text{ (by axiom A5)} \\ [X = 1] \rightarrow 1 \cdot 1 = 1 \text{ (by axiom A4)} \end{array} \right.$

Proof

Hence, $X \cdot 1 = X$.

Two (and Three) Variable Theorems

$$(T6) X + Y = Y + X$$

$$(T6') XY = YX$$

(Commutativity)

$$(T7) (X + Y) + Z = X + (Y + Z)$$

$$(T7') (XY)Z = X(YZ)$$

(Associativity)

$$(T8) XY + XZ = X(Y + Z)$$

$$(T8') (X + Y)(X + Z) = X + YZ$$

(Distributivity)

$$(T9) X + XY = X$$

$$(T9') X(X + Y) = X$$

(Covering)

$$(T10) XY + XY' = X$$

$$(T10') (X + Y)(X + Y') = X$$

(Combining)

$$(T11) XY + X'Z + YZ = XY + X'Z$$

(Consensus)

$$(T11') (X + Y)(X' + Z)(Y + Z) = (X + Y)(X' + Z)$$

Adsorption Theorem (not in the textbook):


$$(T^*) X + X'Y = X + Y \quad (T^*)' X(X' + Y) = XY$$



All theorems can be proved, either *algebraically* or through the use of a *truth table*.

Example: Proof by Truth Table

- Show that ...
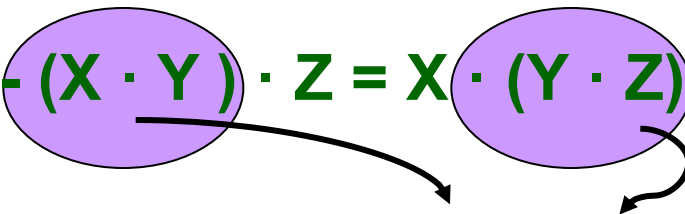
$$(T7') \quad (X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$$


X	Y	Z	XY	YZ	(XY)Z	X(YZ)
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	1	0	0
1	0	0	0	0	0	0
1	0	1	0	0	0	0
1	1	0	1	0	0	0
1	1	1	1	1	1	1

Theorems (T8) – (T11)

- **Theorem (T8)** may be used to convert a *product of sums* expression to a *sum of products* expression.
- **Theorem (T8')** is often used to convert a *sum of products* expression to a *product of sums* expression.
- **Theorems (T9), (T10), and (T11)** are often used to **minimise** (or *simplify*) **a logic circuit**.
 - **Shared property** by these theorems: there is a reduction in the number of logic gates from left to right.



Examples of this later on!

N Variable Theorems

- **Two or three variables' theorems can be extended** to an arbitrary number of variables, **N**:

- **Generalised Idempotency**

$$(T12) \quad X + X + \dots + X = X$$

$$(T12') \quad X \cdot X \cdot \dots \cdot X = X$$



(T14) states: given any *N*variable logic expression, its complement can be obtained by swapping **+** and **·**, and complementing all variables.

- **De Morgan's Theorems**

$$(T13) \quad (X_1 \cdot X_2 \cdot \dots \cdot X_n)' = X_1' + X_2' + \dots + X_n'$$

$$(T13') \quad (X_1 + X_2 + \dots + X_n)' = X_1' \cdot X_2' \cdot \dots \cdot X_n'$$

(T14): condensed form for (T13) & (T13').

- **Generalised De Morgan's Theorem**

$$(T14) \quad [F(X_1, X_2, \dots, X_n, +, \cdot)]' = F(X_1', X_2', \dots, X_n', \cdot, +)$$

- **Shannon's Expansion Theorems**

$$(T15) \quad F(X_1, X_2, \dots, X_n) = X_1 \cdot F(1, X_2, \dots, X_n) + X_1' \cdot F(0, X_2, \dots, X_n)$$

$$(T15') \quad F(X_1, X_2, \dots, X_n) = [X_1 + F(0, X_2, \dots, X_n)] \cdot [X_1' + F(1, X_2, \dots, X_n)]$$

De Morgan: "Break the line and change the sign"

De Morgan's Theorems: Truth Tables

(T13) $(X + Y)' = X' \cdot Y'$

(T13') $(X \cdot Y)' = X' + Y'$

(T13), (T13') for **N=2** variables.


X	Y	X'	Y'	X+Y	(X+Y)'	X'•Y'	X•Y	(X•Y)'	X' + Y'
0	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	0	1	1	0	0	0	1	1
1	1	0	0	1	0	0	1	0	0

Like *Theorem 8*, **De Morgan's law** may be used to convert between a sum of products and a product of sums.

Designing with NAND gates


- Examples:**

INVERTER

 


This is only to simplify the implementation!

AND

 


OR

 

Here, **+** does not represent addition.


NAND Gates: 2 ways to view

- **3-input NAND** gate:

 

is equivalent to

- **3 INVERTED input OR** gate:

 


X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Designing with NOR gates


- Examples:**

INVERTER

 


This is only to simplify the implementation!

OR

 


AND

 


NOR Gates: 2 ways to view

- **3-input NOR** gate:

 

is equivalent to



- **3 INVERTED input AND** gate:

 

X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Exclusive OR Logic Gates: Properties

- XOR** and **XNOR** gates:

  

- Identities:**

$$X \oplus 0 = X$$

$$X \oplus 1 = X'$$

$$X \oplus X = 0$$

$$X \oplus X' = 1$$

$$X \oplus Y' = (X \oplus Y)'$$



$$X' \oplus Y = (X \oplus Y)'$$

$$X \oplus Y = Y \oplus X$$

$$(X \oplus Y) \oplus Z = X \oplus Y \oplus Z$$

XOR & XNOR Gates

  - XOR** and **XNOR** gates can be designed using basic gates (i.e., *inverted input OR gates* and *NAND gates*):



The Principle of Duality

- The **Principle of Duality**:
 - Used in *simplifying logic equations*.
 - Obtain the *dual* by interchanging OR and AND operations.
- **Example**:
 - The dual of $F = X \cdot Y + Z \cdot W$ is $F^D = (X + Y) \cdot (Z + W)$.



Principle of Duality: Not the same as saying the two expressions are equal!

Complements

- How do we ***get the complement of a function?***
 - Can derive the complement of a function algebraically by applying De Morgan's theorem.
 - or***
 - Can obtain via Truth Table by interchanging **1's** and **0's** for the function **F**.
 - or***
 - Can obtain by interchanging **AND** and **OR** operations and complementing each variable.



This is a ***straightforward application of De Morgan's theorem.***

Example: Complement Function

Truth Table

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

Using a Truth
Table to find **F'**.

Find the complement of **F**:

$$\mathbf{F = A'BC' + A'B'C}$$

Step 1: Find the Dual.

$$\mathbf{F^D = (A' + B + C')(A' + B' + C)}$$

Step 2: Complement each variable.

$$\mathbf{F' = (A+B'+C)(A+B+C')}$$

*The result is the
Complement Function!*

Consensus Theorem (T11)

- Useful in simplifying Boolean expressions
 - Allows the elimination of unnecessary terms.

Truth Table

X	Y	Z	F	G
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	0	0
1	1	0	1	1
1	1	1	1	1

Show: $XY + \bar{X}Z + YZ = XY + \bar{X}Z$

$$F = XY + \bar{X}Z + YZ = XY + \bar{X}Z + YZ(\underbrace{X + \bar{X}}_{=1})$$

expand

$$= XY + \bar{X}Z + XYZ + \bar{X}YZ$$

reorder

$$= XY + XYZ + \bar{X}Z + \bar{X}YZ$$

factorise

$$= XY(\cancel{1 + Z}) + \bar{X}Z(\cancel{1 + Y})$$

$$G = XY + \bar{X}Z$$

$\therefore YZ$ is an unnecessary (or redundant) term

Example (1/3): Two Equations

- Show that $F_1 = F_2$ using a Truth Table.

$$F_1 = X' \cdot Y' \cdot Z + X' \cdot Y \cdot Z + X \cdot Y'$$

$$F_2 = X' \cdot Z + X \cdot Y'$$




To prove the equality, we can use Switching Algebra theorems **T8 + T5**.

X	Y	Z	F_1	F_2
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	0	0
1	1	1	0	0

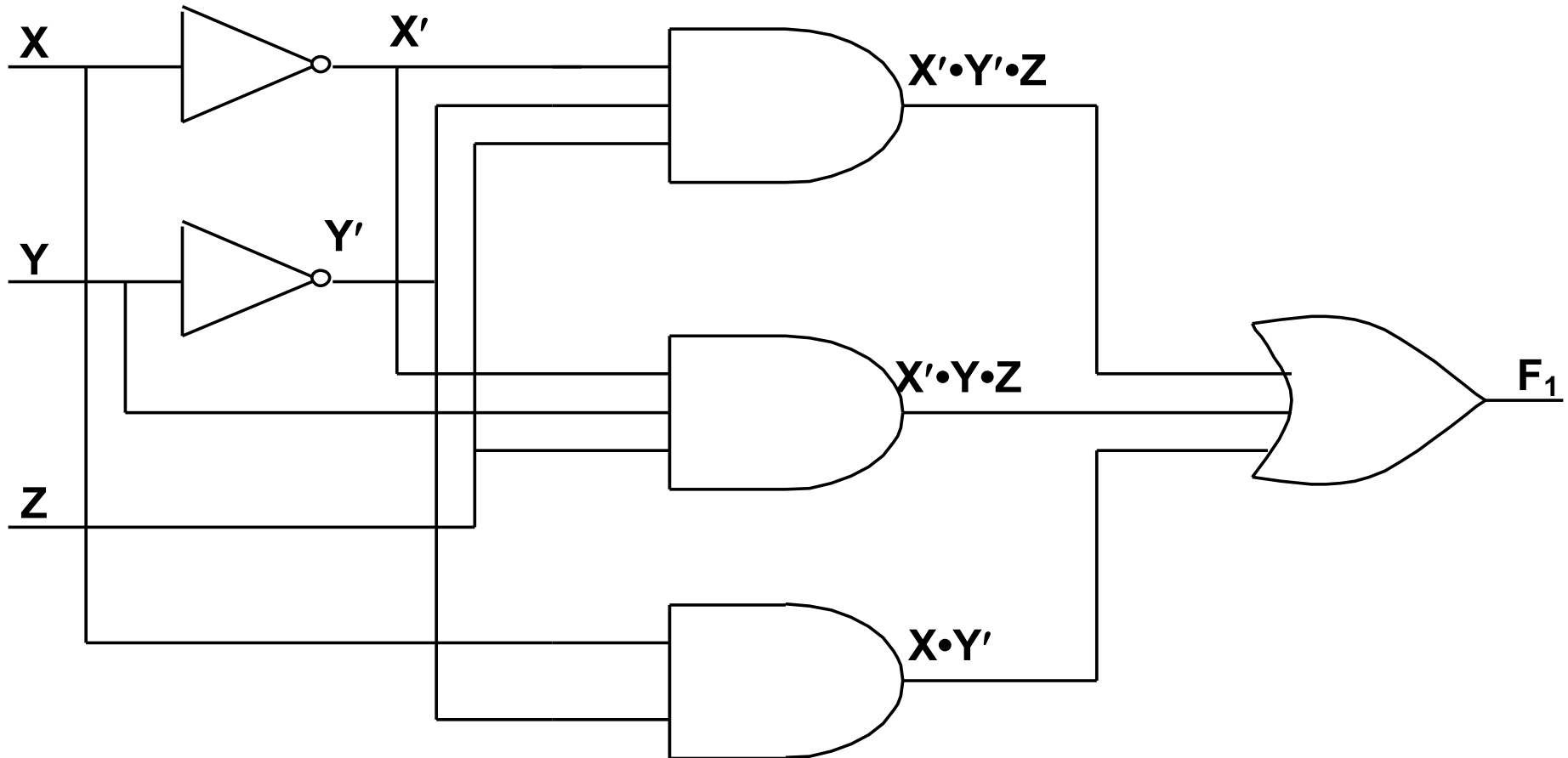Example (2/3): Two Equations

$$F_1 = X' \cdot Y' \cdot Z + X' \cdot Y \cdot Z + X \cdot Y'$$



Example (3/3): Two Equations

To be completed in class ...

$$F_2 = X' \cdot Z + X \cdot Y'$$

Example 1: Minimisation

$$F = A'B'C + AB'C$$



(T10) – Combining Theorem

$$F = B'C$$



How is (T10) applied here?

Alternatively, if we were to factor **A** out, it would have left us with:

$$F = B'C(A' + A) \quad (\text{using T8})$$

$$A' + A = 1 \quad (\text{using T5})$$

therefore, $F = B'C$

Example 2: Minimisation (1)

$$F = A'B'C' + A'B'C + A'BC$$

$$A'B'C = A'B'C + A'B'C$$

$$(T3) \quad X + X = X$$



$$F = A'B'C' + A'B'C + A'B'C + A'BC$$

T10

T10

$$F = A'B' + A'C$$

$$(T10) \quad XY + XY' = X$$



Circuit Diagrams for these functions?

Example 2: Minimisation (2)

To be completed in class ...

$$F = A'B'C' + A'B'C + A'BC$$

$$F = A'B' + A'C$$

Example: Minimisation of F

$$\text{Simplify } F = (AB'(A + C))' + A'B(A + B' + C)'$$

$$= (AB' + AB'C)' + A'B(A + B' + C)'$$

MULTIPLY
THROUGH
TERM 1
APPLYING
(T3') $X \cdot X = X$

APPLY (T13') to
 $(AB' + AB'C)'$ &
 $(A + B' + C)'$

$$\longrightarrow = (A' + B)(A' + B + C') + A'B(A'BC')$$

EXPAND TERMS

$$\left\{ \begin{aligned} &= (A' + B)(A' + B + C') + A'BC' \\ &= A'A' + A'B + A'C' + BA' + BB + BC' + A'BC' \end{aligned} \right.$$

$$\text{APPLY (T3')} \longrightarrow = A' + A'B + A'C' + BA' + B + BC' + A'BC'$$

$$\text{APPLY (T1')} \longrightarrow = A'(1 + B + C' + B + BC') + B(1 + C')$$

$$\text{APPLY (T2)} \longrightarrow = A'(1) + B(1)$$

$$= A' + B$$

Logic Functions (1/2)

- Logic Functions' Representations:
 - **Truth Table**: practical only for a small number of variables.
 - **Algebraic sum of minterms** (*Canonical Sum*):
 - **minterm**: a product of n distinctive logic variables (or their complements); e.g., $X \cdot Y \cdot Z$;
 - the **sum of minterms** corresponds to the combination of Truth Table rows for which the function produces a **1** output;
 - for a **n -variable** logic function, each **minterm** must consist of n variables and within each **minterm**, each variable is represented by its complement if the variable value is **0**.

Logic Functions (2/2)

- Logic Functions' Representations (cont.):
 - **Algebraic product of maxterms** (*Canonical Product*):
 - **maxterm**: is the sum of n distinctive logic variables or their complements e.g., $X+Y+Z$;
 - the **product of maxterms** corresponds to the product of Truth Table rows for which the function produces a **0** output;
 - for a **n -variable** logic function, each **maxterm** must consist of n variables and within each **maxterm**, each variable is represented by its complement if the variable value is **1**.

Minterms & Maxterms for 3 Variables

X	Y	Z	Product Term	Symbol	Sum Term	Symbol
0	0	0	$\overline{X} \cdot \overline{Y} \cdot \overline{Z}$	m_0	$X+Y+Z$	M_0
0	0	1	$\overline{X} \cdot \overline{Y} \cdot Z$	m_1	$X+Y+\overline{Z}$	M_1
0	1	0	$\overline{X} \cdot Y \cdot \overline{Z}$	m_2	$X+\overline{Y}+Z$	M_2
0	1	1	$\overline{X} \cdot Y \cdot Z$	m_3	$X+\overline{Y}+\overline{Z}$	M_3
1	0	0	$X \cdot \overline{Y} \cdot \overline{Z}$	m_4	$\overline{X}+Y+Z$	M_4
1	0	1	$X \cdot \overline{Y} \cdot Z$	m_5	$\overline{X}+Y+\overline{Z}$	M_5
1	1	0	$X \cdot Y \cdot \overline{Z}$	m_6	$\overline{X}+\overline{Y}+Z$	M_6
1	1	1	$X \cdot Y \cdot Z$	m_7	$\overline{X}+\overline{Y}+\overline{Z}$	M_7

Minterms



Maxterms

A *minterm* and a *maxterm* with the same subscript number are complements of each other: $M_0 = \overline{m_0}$

Representing a Function in *Standard Form*

A **Boolean Function** can be expressed algebraically from a given Truth Table by forming the logical sum of all **minterms** which produce a '**1**' in the function.

Truth Table

X	Y	Z	F	\bar{F}	
0	0	0	1	0	m_0
0	0	1	0	1	m_1
0	1	0	1	0	m_2
0	1	1	0	1	m_3
1	0	0	0	1	m_4
1	0	1	1	0	m_5
1	1	0	0	1	m_6
1	1	1	1	0	m_7

F = 1 for each of the combinations of variables:
 $X' \cdot Y' \cdot Z'$, $X' \cdot Y \cdot Z'$, $X \cdot Y' \cdot Z$, $X \cdot Y \cdot Z$.

So: $F = X' \cdot Y' \cdot Z' + X' \cdot Y \cdot Z' + X \cdot Y' \cdot Z + X \cdot Y \cdot Z$
 $F = m_0 + m_2 + m_5 + m_7 = \Sigma m(0, 2, 5, 7)$

And: $F' = m_1 + m_3 + m_4 + m_6 = \Sigma m(1, 3, 4, 6)$

$$F'' = (m_1 + m_3 + m_4 + m_6)'$$

$$F'' = m_1' \cdot m_3' \cdot m_4' \cdot m_6'$$

$$F = M_1 \cdot M_3 \cdot M_4 \cdot M_6 = \prod M(1, 3, 4, 6)$$

Minterms & Sum of Products

- Properties of *Minterms*:
 - There are 2^n minterms for n Boolean variables.
 - Any Boolean function can be expressed as a logical sum of *minterms*.
 - A function's complement contains those *minterms* not included in the original function.
 - A function that includes all the 2^n *minterms* is always equal to logic value 1 .
- Sum of Products' Expressions:
 - Similar to *sum of minterms*, but the *sum of products* is in simplified form and may not contain all the variables in each expression.
 - Used in design process to achieve solutions with minimum gate counts.

Example: Sum of Products & Simplification (1/2)



A Boolean Function in **Sum of Minterms** form can be simplified to a **Sum of Products** form by algebraic manipulation or map simplification.

Truth Table

X	Y	Z	F	
0	0	0	1	m_0
0	0	1	1	m_1
0	1	0	1	m_2
0	1	1	0	m_3
1	0	0	1	m_4
1	0	1	1	m_5
1	1	0	0	m_6
1	1	1	0	m_7

$F = 1$ for each of the combinations of variables:
 $X' \cdot Y' \cdot Z'$, $X' \cdot Y' \cdot Z$, $X' \cdot Y \cdot Z'$, $X \cdot Y' \cdot Z'$, $X \cdot Y' \cdot Z$

So:

$$F = X' \cdot Y' \cdot Z' + X' \cdot Y' \cdot Z + X' \cdot Y \cdot Z' + X \cdot Y' \cdot Z' + X \cdot Y' \cdot Z$$

$$F = \Sigma m(0, 1, 2, 4, 5)$$

- F can be simplified by algebraic or map
- simplification techniques to a **Sum of Products**.

Example: Sum of Products & Simplification (2/2)



Which equation is easier to build?

$$F = X' \cdot Y' \cdot Z' + X' \cdot Y' \cdot Z + X' \cdot Y \cdot Z' + X \cdot Y' \cdot Z' + X \cdot Y' \cdot Z$$

T10

T10

$$F = X' \cdot Y' + X' \cdot Y \cdot Z' + X \cdot Y'$$

T10

$$F = Y' + X' \cdot Y \cdot Z'$$

T* (Adsorption Theorem)

$$F = Y' + X' \cdot Z'$$



Simplification of **F** using algebraic manipulation.

Minterm & Maxterm Expansions of F , F'

Example for $F(X, Y, Z)$: 2^3 terms (numbered 0 through to 7).

Given Form	Minterm Expansion of F	Maxterm Expansion of F	Minterm Expansion of F'	Maxterm Expansion of F'
$F = \sum m(3,4,5,6,7)$	–	$\prod M(0,1,2)$	$\sum m(0,1,2)$	$\prod M(3,4,5,6,7)$
$F = \prod M(0,1,2)$	$\sum m(3,4,5,6,7)$	–	$\sum m(0,1,2)$	$\prod M(3,4,5,6,7)$

Expansion into Canonical SOP & POS

- How to **expand Boolean function into canonical SOP**:
 - Use properties (T1') and (T5).
 - Take each *product term* with a missing literal variable (e.g., A) and **AND** it (logic operation) with the *sum term* ($A + A'$).

- How to **expand Boolean function into canonical POS**:
 - Use the *distributive property* i.e., (T8').
 - Take each *sum term* with a missing literal variable (e.g., A) and **OR** it (logic operation) with the *product term* ($A.A'$).

Example: Sum of Products

Problem: Expand the boolean function $F(A,B,C) = A'B' + BC$ into a standard *sum of products* (aka *minterm expansion*, *canonical SOP*).

$$\begin{aligned} F(A,B,C) &= A'B' + BC \\ &= A'B'(C+C') + BC(A+A') \quad \text{by (T5), (T1')} \\ &= A'B'C + A'B'C' + ABC + A'BC \quad \text{by (T8), (T6), (T6')} \end{aligned}$$

To get the Σm expression, replace all *normal literals with a 1* and all *primed literals with a 0*: (**Example:** $A'B'C \Rightarrow A' = 0, B' = 0, C = 1 \Rightarrow 001$).

$$F(A,B,C) = \Sigma m(001, 000, 111, 011)$$

Now convert to decimal (and put them in order), $F(A,B,C) = \Sigma m(0, 1, 3, 7)$.

Example: Product of Sums

Problem: Expand the boolean function $F(A,B,C) = A'B' + BC$ into a standard *product of sums* (aka *maxterm expansion*, *canonical POS*).

$$\begin{aligned} F(A,B,C) &= A'B' + BC \\ &= (A'B' + B)(A'B' + C) \quad \longrightarrow \text{by variable substitution, (T8')} \\ &= (A' + B)(B' + B)(A' + C)(B' + C) \text{ by (T8')} \\ &= (A' + B + CC')(A' + C + BB')(B' + C + AA') \text{ by (T1), (T5')} \\ &= (A' + B + C)(A' + B + C')(A' + C + B)(A' + C + B')(B' + C + A)(B' + C + A') \\ &= (A' + B + C)(A' + B + C')(A' + B' + C)(A + B' + C) \text{ by (T3'), (T6)} \end{aligned}$$

To get the ΠM expression replace all *normal literals* with a 0 and all *primed literals* with a 1: (**Example:** $A' + B' + C \Rightarrow A' = 1, B' = 1, C = 0 \Rightarrow 110$).

$$F(A,B,C) = \Pi M(100, 101, 110, 010)$$

Now convert to decimal (and order them): $F(A,B,C) = \Pi M(2, 4, 5, 6)$.

Deriving the Standard *Product of Sums* Expression

- Remember:** If you are unsure of your answer, you can check it with a Truth Table; fill in Truth Table as per original $F = A'B' + BC$!

For: F' (*minterms*) or
 F (*maxterms*) where $F = 0$.



Does our expression have all the terms indicated by the Truth Table?

$$F = (A'+B+C)(A'+B+C') \cdot (A'+B'+C)(A+B'+C)$$

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

For: F (*minterms*) or F' (*maxterms*) where $F = 1$.