



Queen Mary

University of London

Science and Engineering

EBU4202: Digital Circuit Design

Tutorial Block 3

Dr. Md Hasanuzzaman Sagor (Hasan)

Dr. Chao Shu (Chao)

Dr. Farha Lakhani (Farha)


School of Electronic Engineering and Computer Science,
Queen Mary University of London,
London, United Kingdom.

Tutorials Block 3_2024

Q1. Draw the circuit diagram of a SR Latch with Control Input using only NAND gates.

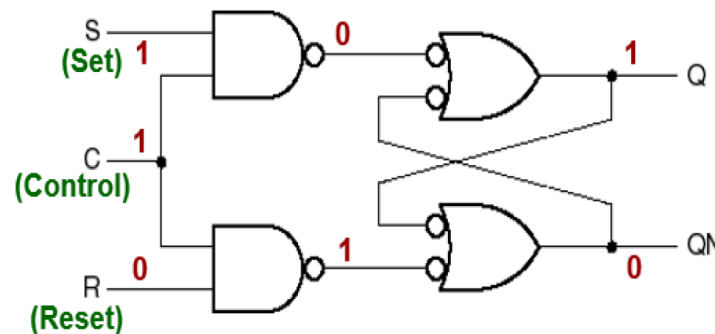Q2. Consider the circuit shown in Figure 2. Answer the following questions:


- What is the name for this type of flip-flop?
- Imagine that S now goes low. $R = 0$ and $C = 1$. Use your knowledge of the operation of gates to determine the new values of Q and QN
- Imagine that C now goes low. $S = 0$ and $R = 1$. Use your knowledge of the operation of gates to determine the new values of Q and QN
- Imagine that C now goes high. $S = 1$ and $R = 0$. Use your knowledge of the operation of gates to determine the new values of Q and QN



Tutorials Block 3_2024

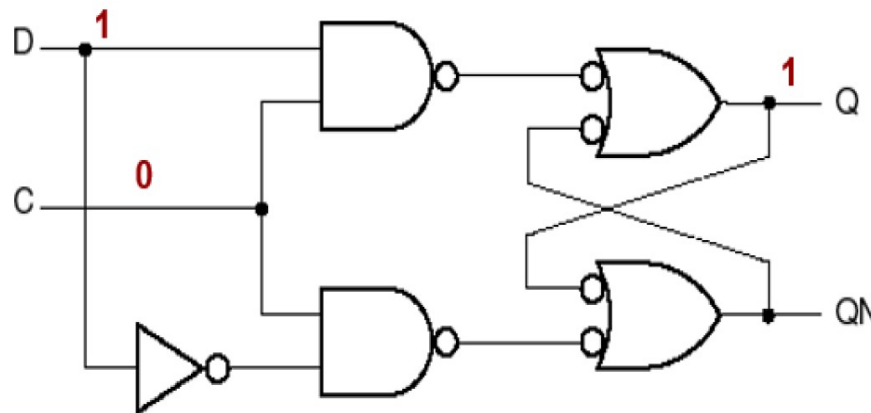Q3. Consider the circuit shown in Figure 3. Answer the following questions:

- What is the name for this type of sequential circuit?
- Imagine that C now goes high. $D = 1$. Use your knowledge of the operation of gates to determine the new values of Q and QN
- Imagine that D now goes low. $C = 1$. Use your knowledge of the operation of gates to determine the new values of Q and QN
- Imagine that C now goes low. $D = 1$. Use your knowledge of the operation of gates to determine the new values of Q and QN



Tutorials Block 3_2024

Q4. What is a synchronous state machine?

Q5. In the context of bistable elements and state machines, what is meant by the term “metastability”?

Q6. Explain the difference between a Moore and Mealy machine.

Q7. What is the maximum clock frequency for a circuit having a maximum delay T_D ? How can the circuit become unstable?

Tutorials Block 3_2024

Q8. Answer the following questions about the sequential circuit:

- Derive the **input**, **next state** and **output equations**.
- Derive the **State Table** and **State Diagram**.
- What does the circuit do?

