

Beijing University of Posts and Telecommunications,
Changping , Beijing, China

JUNE 6,2015
MR.Li Yonghua
BUPT, Haidian
Beijing, China

LABORATORY REPORT

INTEGRAL AND DIFFERENTIATING CIRCUIT

INTRODUCTORY SUMMARY

Last week we do the 5th experiment in circuit lab. The laboratory is about integral and differentiating circuit and the aim of the experience are

1. Learn to use operational amplifier composing integral differentiating circuit.
2. Grasp the characteristic and the performance of the integral differentiating circuit.

After do the experiment I check the data and summery the conclusion and finally finish this report.

LAB EQUIPMENT

- Digital multitester
- DC stabilized voltage power supply
- Function signal generating device
- AC millivolt
- Double-trace oscilloscope

LAB PROCEDURE

This laboratory contains three parts including integral circuit, differentiating circuit and integral-differentiating circuit.

1. Integral circuit

Experimental circuit is as shown in Figure 1. Analyze Figure 1 circuit, think if the input is sine wave, how many u_o and u_i phase difference are. And when the input signal is 100HZ, RMS value is 2V, count the outputs u_o .

- 1.1 Taking $u_i = -1V$, separate switch K (switch K replaces with a wire, draws out a wire-port as switch) and observe u_o changes with the oscilloscope.
- 1.2 Measure the saturated output voltage and the effective integral time.
- 1.3 Cause Figure 1 integral capacity to change 0.1 μF , separate K, u_i respectively inputs the 100HZ, amplitude value is the 2V square-wave and the sine wave signal, observe u_i and u_o value and the phase relation, and record the waveform.

1.4 Change Figure 1 circuit's frequency and observe the relations of u_i and u_o phase and amplitude value.

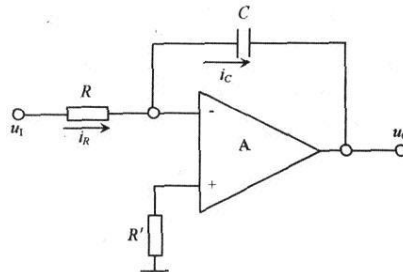


Figure 1

2. Differentiating circuit

Experimental circuit is as shown in Figure 2. Analyze Figure 2 circuit, think if the input is square wave, how many u_o and u_i phase difference are. And when the input signal is 160HZ, amplitude value is 1V, count the outputs u_o .

2.1 The input is sine wave signal $f=160$ HZ and RMS value as 1 V, observe u_i and u_o phase, amplitude value change with the oscilloscope, and record these waveforms.

2.2 Change sine wave frequency(20~400 Hz), observe u_i and u_o phase and amplitude value change with the oscilloscope, and record these waveforms.

2.3 The input is square wave signal, $f=200$ Hz, $u_i=5$ V or -5 V, observe u_i and u_o waveform with the oscilloscope, repeatedly do the above experiment.

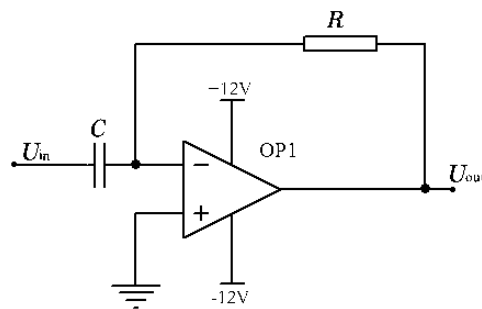


Figure 2

3. Integral-differential circuit

Experimental circuit is as shown in Figure 3.

3.1 u_i input $f=200$ Hz, $U=6$ V or -6 V square signal, observe u_i and u_o waveform with the oscilloscope, and record these waveforms.

3.2 Change $f=500$ Hz and repeatedly do the above experiment.

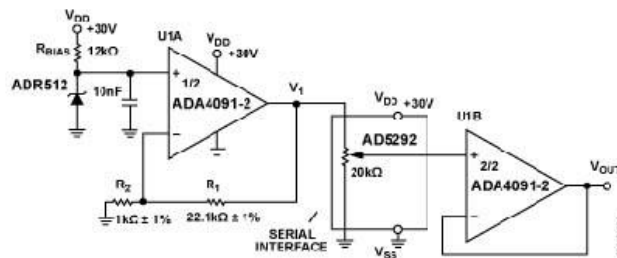


Figure 3

CONCLUSION

From this laboratory I have the conclusion.

1. The integration circuit may be a square wave input is converted into a triangular wave or a time constant of the integrating circuit the ramp.
2. The resistors connected in series in the main circuit, the capacitor trunk.
3. differential circuit allows the input square wave is converted into a sharp pulse wave .
4. The differential circuit capacitors in series in the main circuit, the resistance in the trunk of the time constant of the differentiating circuit.
5. The differential circuit input and output into a differential relationship.

Guo Ruihan
Student