



Queen Mary

University of London

Science and Engineering

## **EBU4202: Digital Circuit Design**

### **Latches and Flip-Flops**

Dr. Md Hasanuzzaman Sagor (Hasan)


Dr. Chao Shu (Chao)

Dr. Farha Lakhani (Farha)

School of Electronic Engineering and Computer Science,  
Queen Mary University of London,  
London, United Kingdom.


# Overview: Sequential Logic Design Principles

- \* Introduction
- \* Bistable Elements
- \* Latches & Flip-Flops
- \* Analysis Procedure
- \* Design Procedure

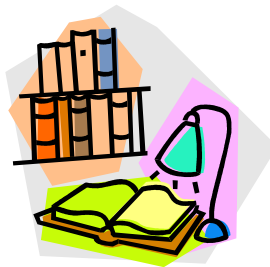


**Chapter 7** – “Digital Design: Principles and Practices” book

# Sequential Circuits (1/2)

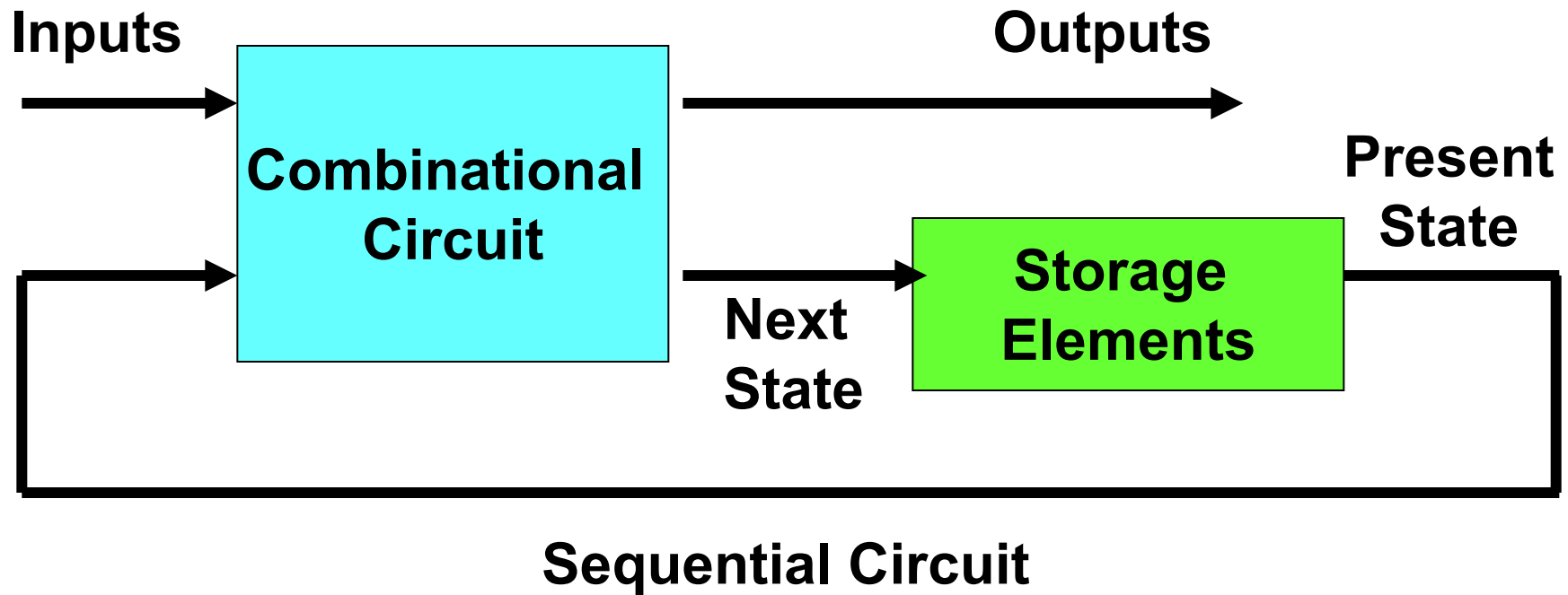

# Sequential Circuits (2/2)

- **Sequential systems** consist of *combinational circuits* and some form of *memory*.
- **Memory** can be either:
  - conventional memory devices; **or**
  - some type of feedback or delay network that serves in place of memory.
- **Examples** of **sequential circuits**:
  - Traffic Lights;
  - elevator controller.



Can you think of  
**other examples?**

# Synchronous vs Asynchronous

- *Sequential systems* come in two basic forms:
    - **Synchronous** → The system's behavior can be defined from the knowledge of its signals at *discrete moments in time*.
    - **Asynchronous** → The behavior depends on the order in which inputs change and can be affected at *any instant of time*.
1. **How** do you think synchronisation is achieved?
  2. **What** do you think may happen with asynchronous systems?

# State

- **State**: The state or characteristics of a circuit are described by the values of its outputs.
  - Given a circuit with  $N$  outputs, with each taking on a binary value, the circuit has a total of  $2^N$  possible states.
  - A state can be *stable* or *metastable*.
- For a sequential circuit, given the current state and input, we can predict the next state.

**Sequential circuits**: also called **FSMs** (Finite State Machines).


# Clock Signals (1/2)

- **Characteristics of a clock signal:**
  - Most sequential circuits undergo a **state change** by a clock signal.
  - A clock signal may be *active high* or *active low*.
  - Its possible states include *high*, *low*, *rising edge*, *falling edge*.
  - Its parameters include *period*, *frequency*, and *duty cycle*.

**Period:** time between successive transitions in the same direction.

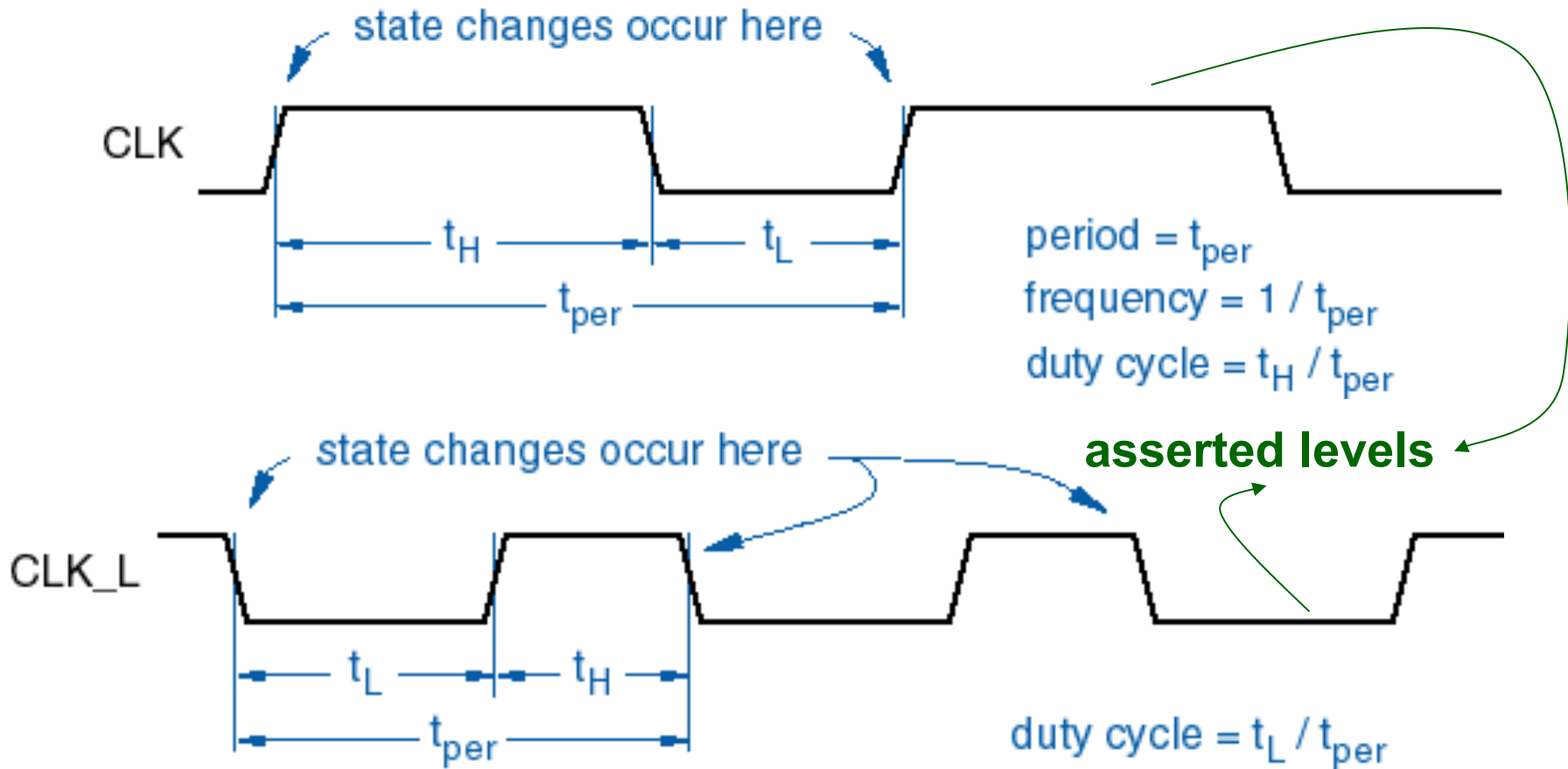
# Clock Signals (2/2)

- Graphical illustration of a clock signal's operation:**






# Synchronous Clocked Sequential Circuit

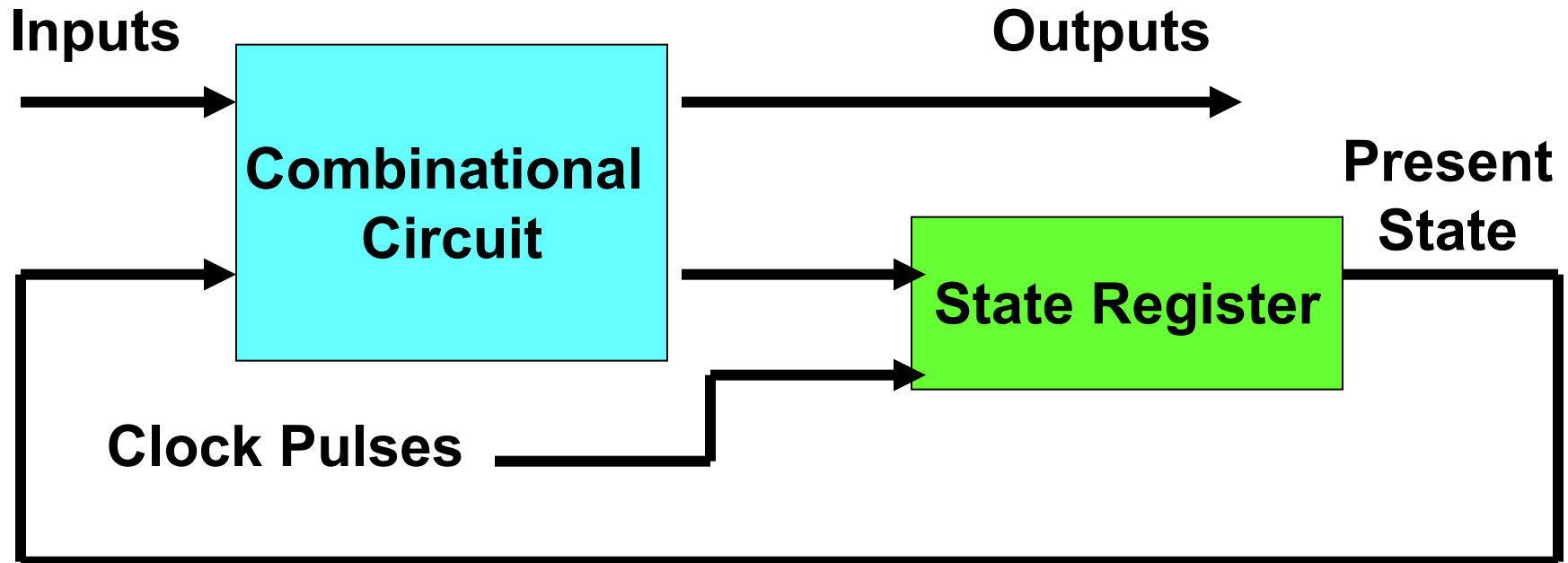


**Timing Diagram of Clock Pulses**

# Gate Delays and Time Diagrams

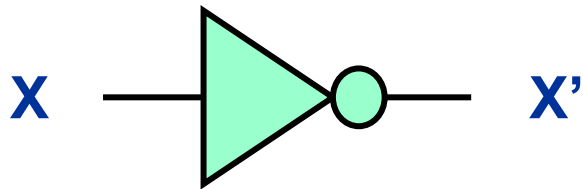


$\epsilon_1$  may be different from  $\epsilon_2$ , why?

 
Q. What does **Propagation Delay** depend on?



# Oscillating Circuit: Not Stable

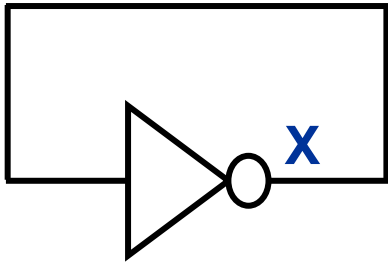



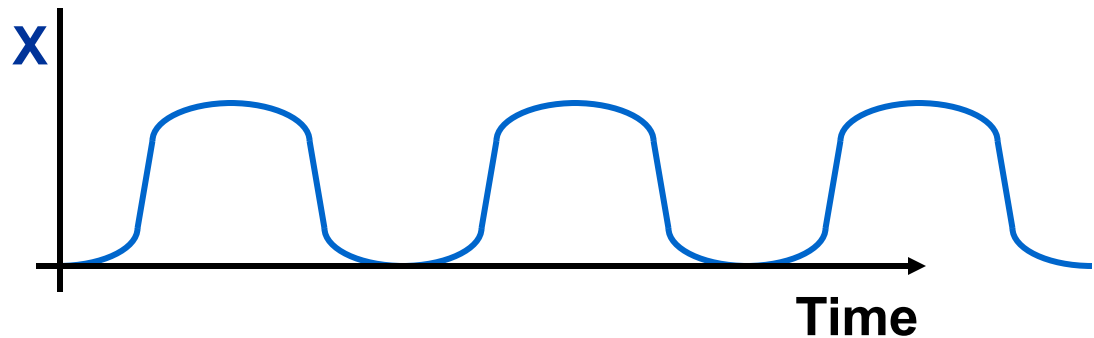
What does “**propagation delay**” depend on?



Circuit **never** reaches stability!!


# Feedback Loop

**Simplest bistable feedback circuit.**

   

# Overview: Sequential Logic Design Principles


- \* Introduction
- \* Bistable Elements
- \* Latches & Flip-Flops
- \* Analysis Procedure
- \* Design Procedure

 


**Chapter 7** – “Digital Design: Principles and Practices” book
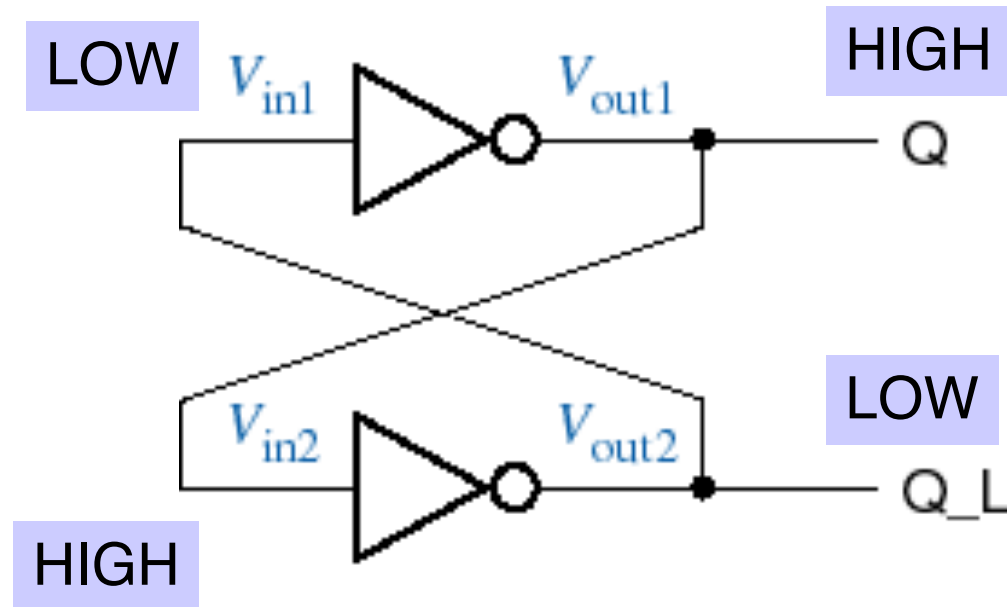
# Bistable Elements (1/2)

- **Bistable Element**: the simplest sequential circuit.
  - Consists of *2 inverters* and has *no inputs* and *2 outputs*.
  - Its *state* is characterised by the *values of its 2 outputs*.
  - It has only *2 states*:  $(1,0)$  or  $(0,1)$ .
  - Its *output* depends only on its *previous input*, through a feedback loop.




# Bistable Elements (2/2)

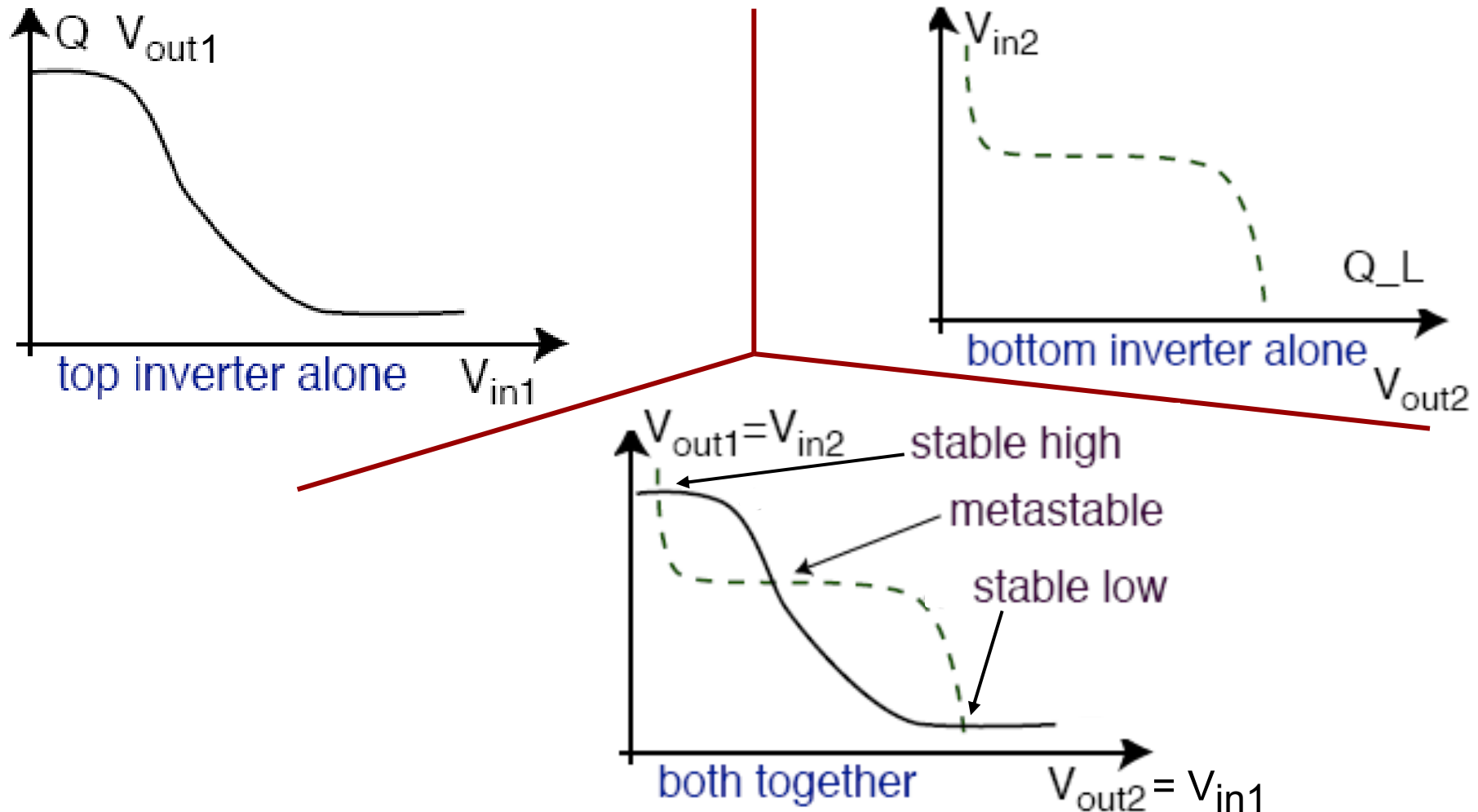
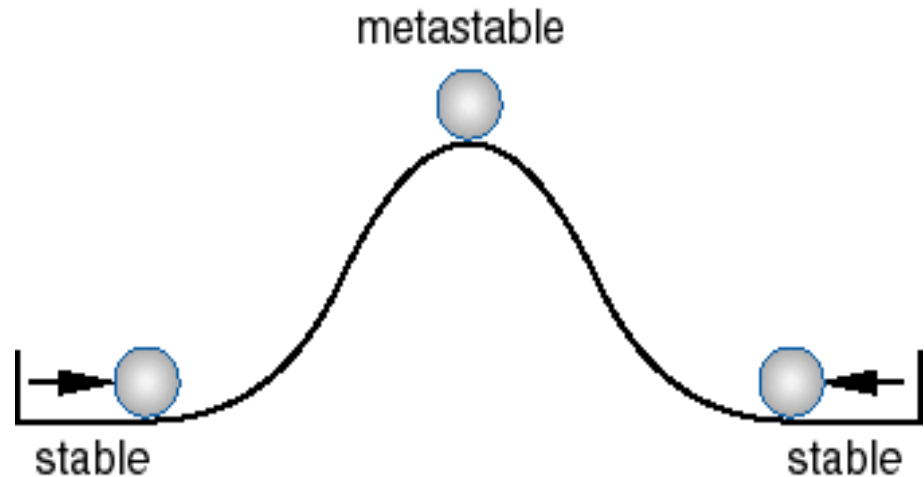
# Metastability & Stable States

- *There are not 2 states, there are 3!*
  - **Metastable** occurs at the point where both inputs are halfway between **0** and **1**.
  - Not a valid state!
  - Could stay in **metastable** forever if it wasn't for noise.





# Metastability: Why is it important?

- **Metastability:**
  - All real systems are subject to it.
    - Problems are caused by “*asynchronous inputs*” that do not meet **flip-flop setup** and **hold times**.
  - Metastability is severe in high-speed systems since clock periods are so short, and “*metastability resolution time*” can be longer than one clock period.
  - Many digital designers, products, and companies have been “burned” by this phenomenon.

# Overview: Sequential Logic Design Principles

- \* Introduction
- \* Bistable Elements
- \* **Latches** & Flip-Flops
- \* Analysis Procedure
- \* Design Procedure



**Chapter 7** – “Digital Design: Principles and Practices” book

# Latches

- **Latch**: Basic storage element from which all *flip-flops* are constructed.
- **Latches** by themselves are not practical for use in synchronous sequential systems:
  - Simple *SR Latches* and *D Latches* do not have control methods to synchronise storage of data elements and therefore cannot be used in synchronous systems.


# Set Reset (SR) Latch

- **SR Latch:**
  - **Undefined state** occurs when both *Set* and *Reset* inputs are **True** (this is “Problematic Design”).
  - Two types: *NOR Gate* and *NAND Gate*.
    - Basically operate in the same way, but use different logic levels to define **truth**.
  - 74 series logic chips: **74LS279**
  - However, **not very practical** for clocked synchronous circuits!


# SR Latch with NOR Gates

**SR Latch:** (1) *S* sets or presets *Q* to 1;  
(2) *R* resets or clears the *Q* output to 0.

**(Reset)**

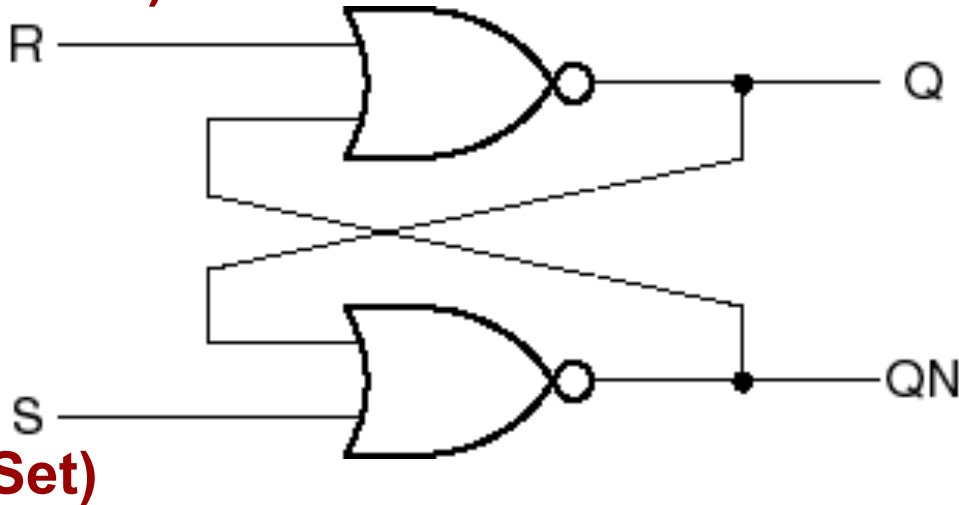

**(Set)**

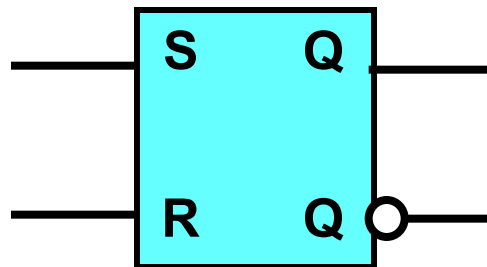


**Inputs**

**Outputs**

S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

Undefined operation  
when both inputs  
are **True**.


# SR Latch Operation (1/2)

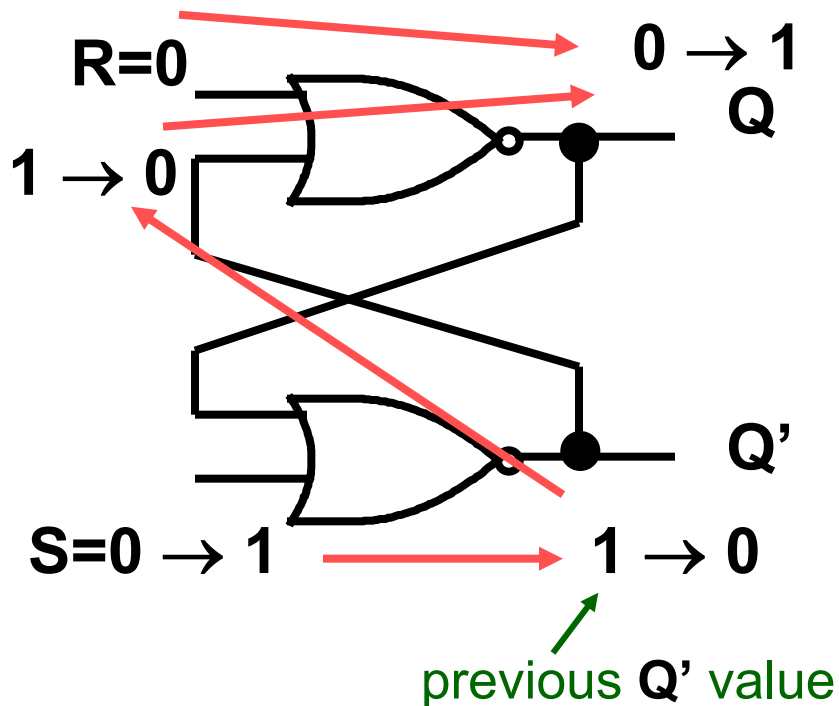

## SET operation

(changing  $S$  to 1)

Initially  $Q = 0$ ;  $Q' = 1$

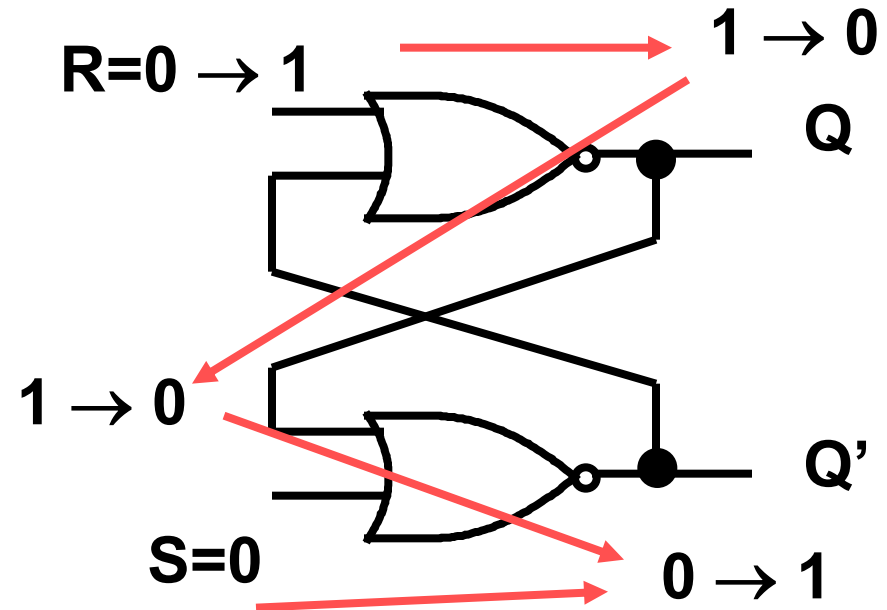


## RESET operation

(changing  $R$  to 1)


Initially  $Q = 1$ ;  $Q' = 0$

# SR Latch Operation (2/2)

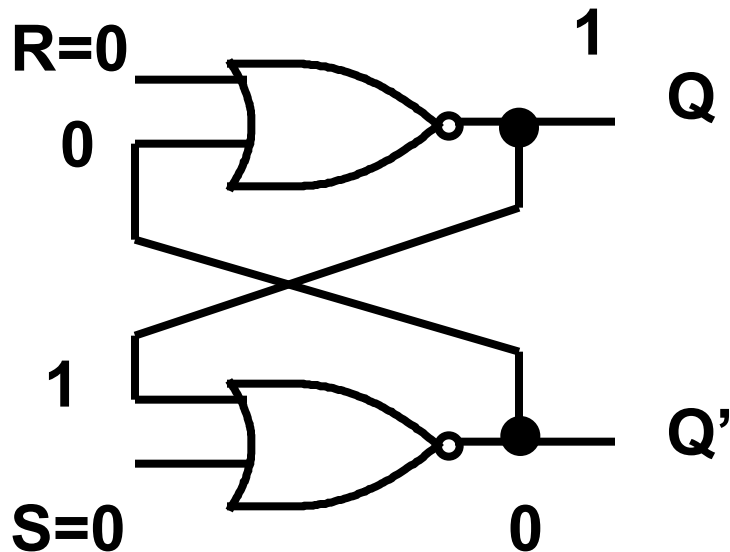

Stable when:

$$S = R = 0, Q = 1$$

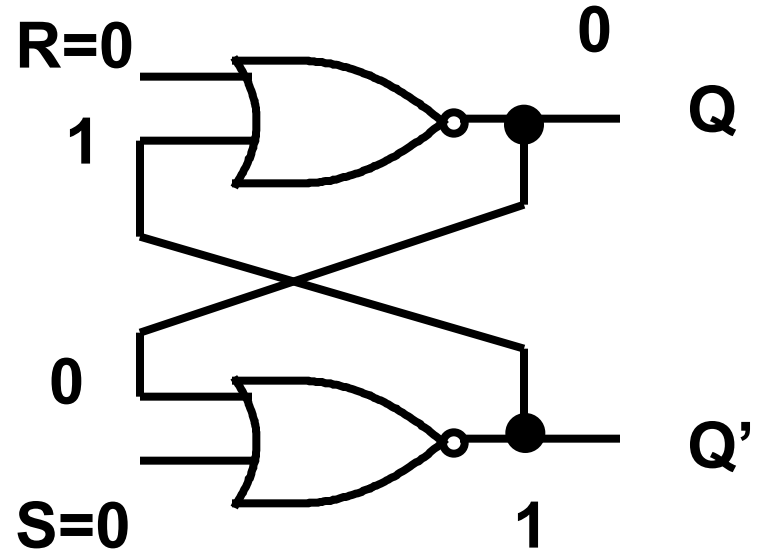


Stable when:

$$S = R = 0, Q' = 1$$
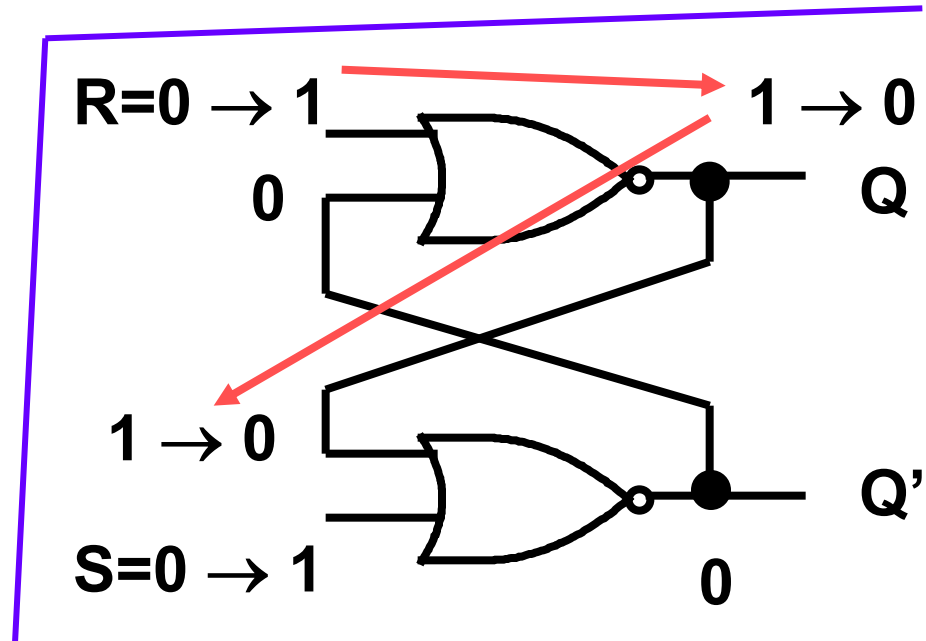
# What about $S = R = 1$ ?


- What happens when both **Set** and **Reset** are **True**?
  - Assume that both  $S$  and  $R$  transition to  $1$  simultaneously.
  - Then,  $Q$  becomes '0', but  $Q'$  remains '0'! So **outputs are no longer complements of each other.**





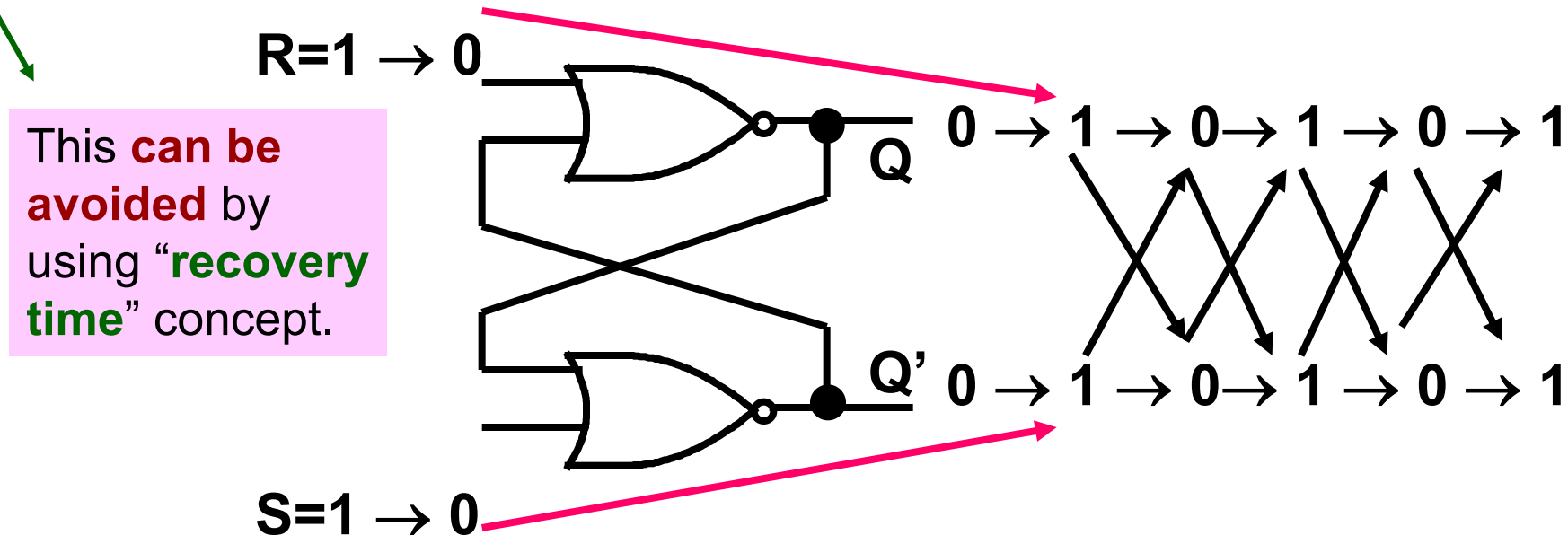
# What happens when $S$ and $R$ return to 0?

- **Oscillation** occurs if both  $S$  and  $R$  return to 0 simultaneously! But at some point, in practical circuit, the system will settle into a stable condition due to the propagation delay.
- The bottom line is that  $S = R = 1$  is an illegal input condition (or the SR latch should be designed, such that one input is **dominant**).




# SR Latch (Built with NAND Gates)

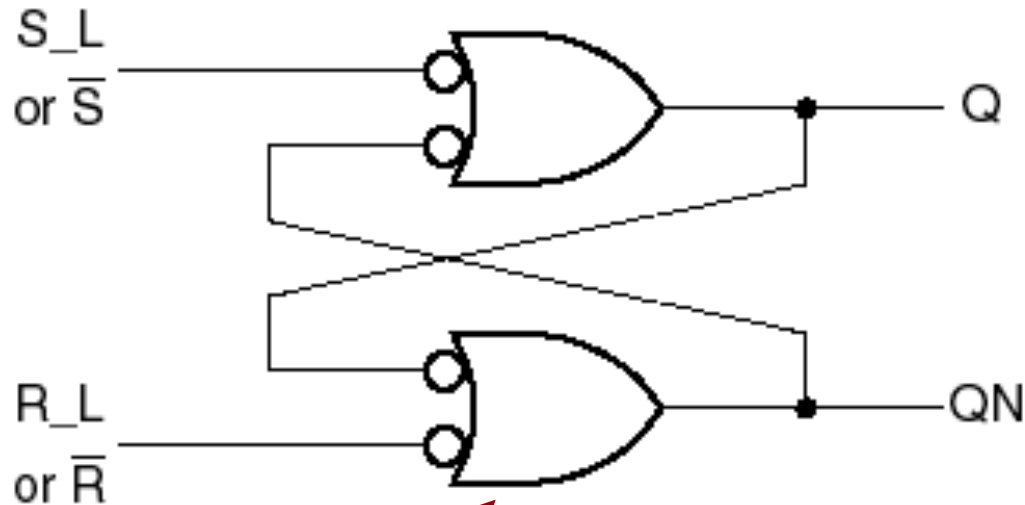

$\bar{S}\bar{R}$  Latch

Same function as  
a **NAND** gate

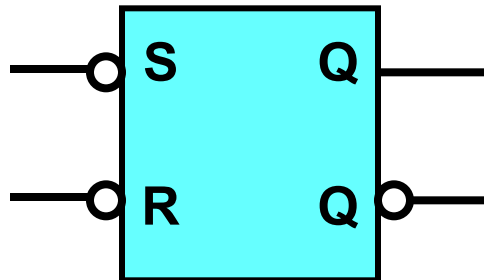

*Inputs*      *Outputs*

S_L	R_L	Q	QN
0	0	1	1
0	1	1	0
1	0	0	1
1	1	last Q	last QN


Undefined operation when  
both inputs are **True**.

# SR Latch with Control Input (1/2)



- What happens if either **Set** or **Reset** are changed in an SR Latch?
  - Must come up with **control method** (**Enable**) to control when SR Latch can be changed.
  - Leaving **Control Line** at logic '0' prevents latch from being written with new value.
  - But **still have** a problem with **indeterminate outputs**!

SR latch with control input: **only sensitive to S, R** inputs when control line is asserted.

# SR Latch with Control Input (2/2)

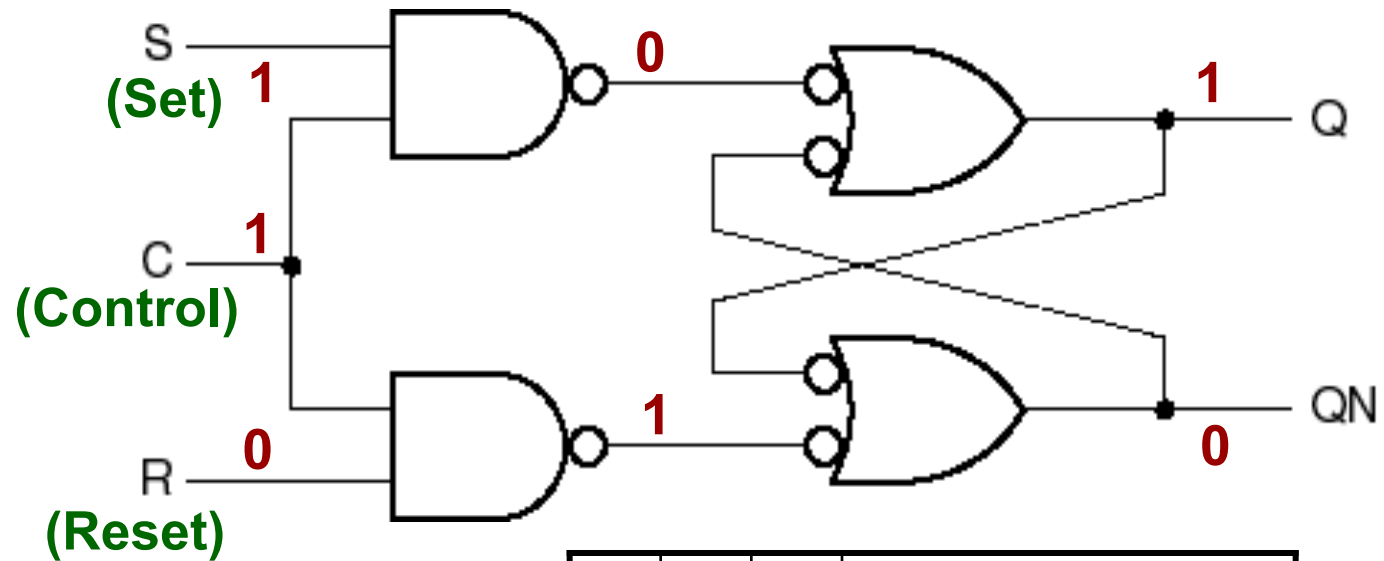

SR Latch  
with Enable

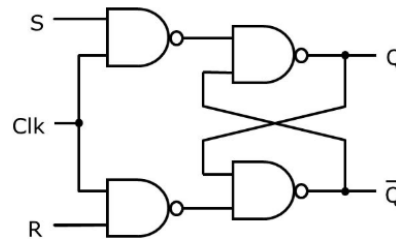 


S	R	C	Q*
0	0	1	
0	1	1	
1	0	1	
1	1	1	
X	X	0	


# D Latch (1/2)

- So far, **we can say**:
  - Don't ever want to design a system where the next state is indeterminate.
  - Can eliminate the **indeterminate state** by ensuring that both **Set** and **Reset** inputs are never equal to '1' at the same time!
- **D Latch**:
  - Has only *two inputs*: **Data** (D) and **Control** (C).
  - *D* input to *Set* input and the complement of *D* input to the *Reset* input always.
  - No longer have an indeterminate state.

# D Latch (2/2)

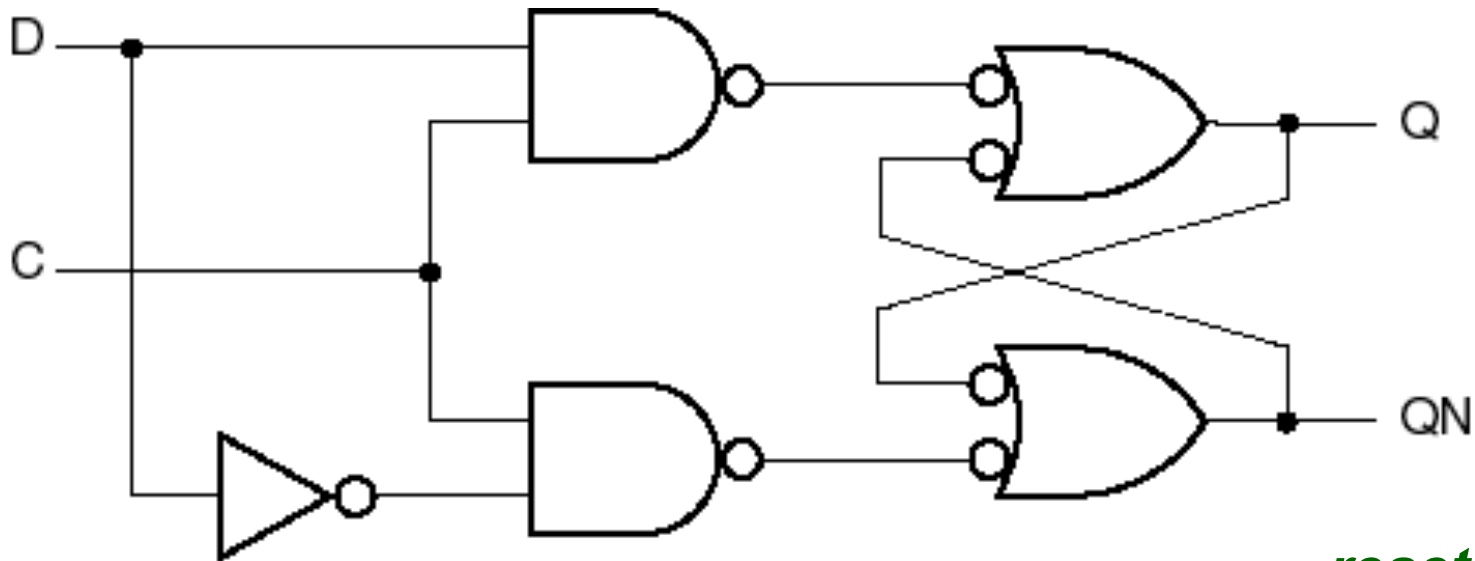

**D Latch**

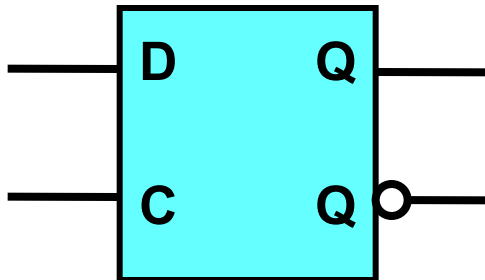


C	D	Q	QN
1	0	0	1
1	1	1	0
0	x	last Q	last QN

*reset state*

*set state*

# D-Latch Operation

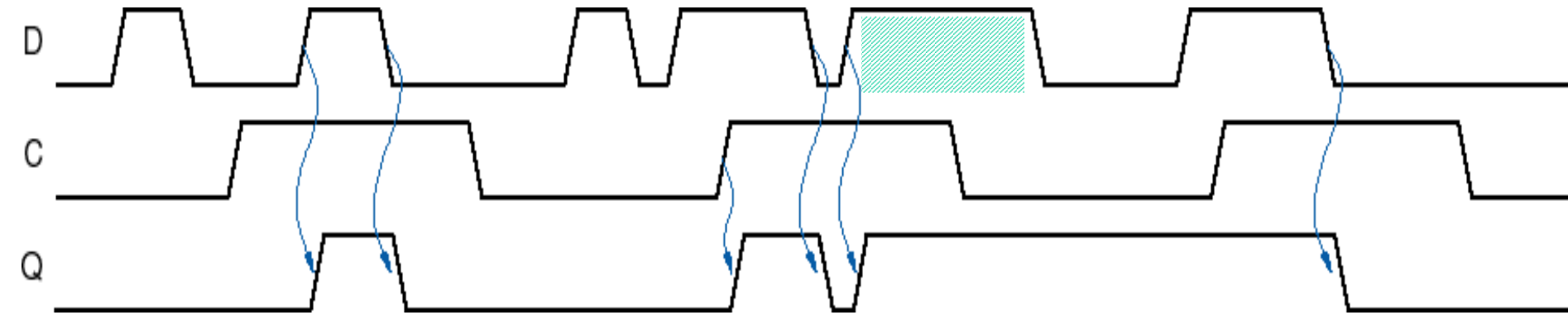


There's a *time window around the falling edge* of **C** when **D** must not change.

# Task 1

- Draw the outputs of an SR latch for the input waveforms shown below.  
Assume that the propagation delay of a NOR gate is 10ns.

$$Q^* = S + R'Q$$

S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

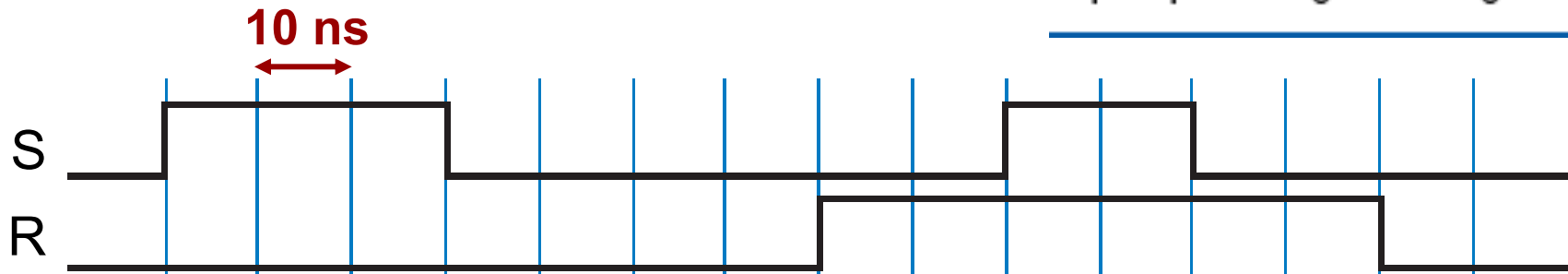

To be completed in class ...





# Overview: Sequential Logic Design Principles

- \* Introduction
- \* Bistable Elements
- \* Latches & Flip-Flops
- \* Analysis Procedure
- \* Design Procedure



**Chapter 7** – “Digital Design: Principles and Practices” book

# Flip-Flops

- **Level sensitive latches** are inadequate, because:
  - Output continually changes if input changes.
  - **Race conditions** can occur.
- Need a better approach to storing data!
  - We will consider both **D and JK-type flip-flops**.
- You can check the following URL for **animated simulation of the various flip-flop types**:

*<http://tams-www.informatik.uni-hamburg.de/applets/hades/webdemos/16-flipflops/10-srff/chapter.html>*


# Master-Slave Flip-Flops

- **How Master-Slave Flip-Flops work:**
  - Employ *two latches*.
  - Isolate output from input:
    - *Output* cannot change continuously with *input*.
    - Input must have a *stable setup time*.



# Master-Slave D Flip-Flop

- Very **popular design tool** (usually present in PLDs).
- Used extensively in designing **registers**.
- Uses **2 D Latches**:
  - *Master D Latch* to latch input.
  - *Slave D Latch* to latch output.
- Latches never operate together.
- Uses **narrow pulse clocking** approach.
- Eliminates racing conditions.



# D Type Master-Slave Flip-Flop (1/5)

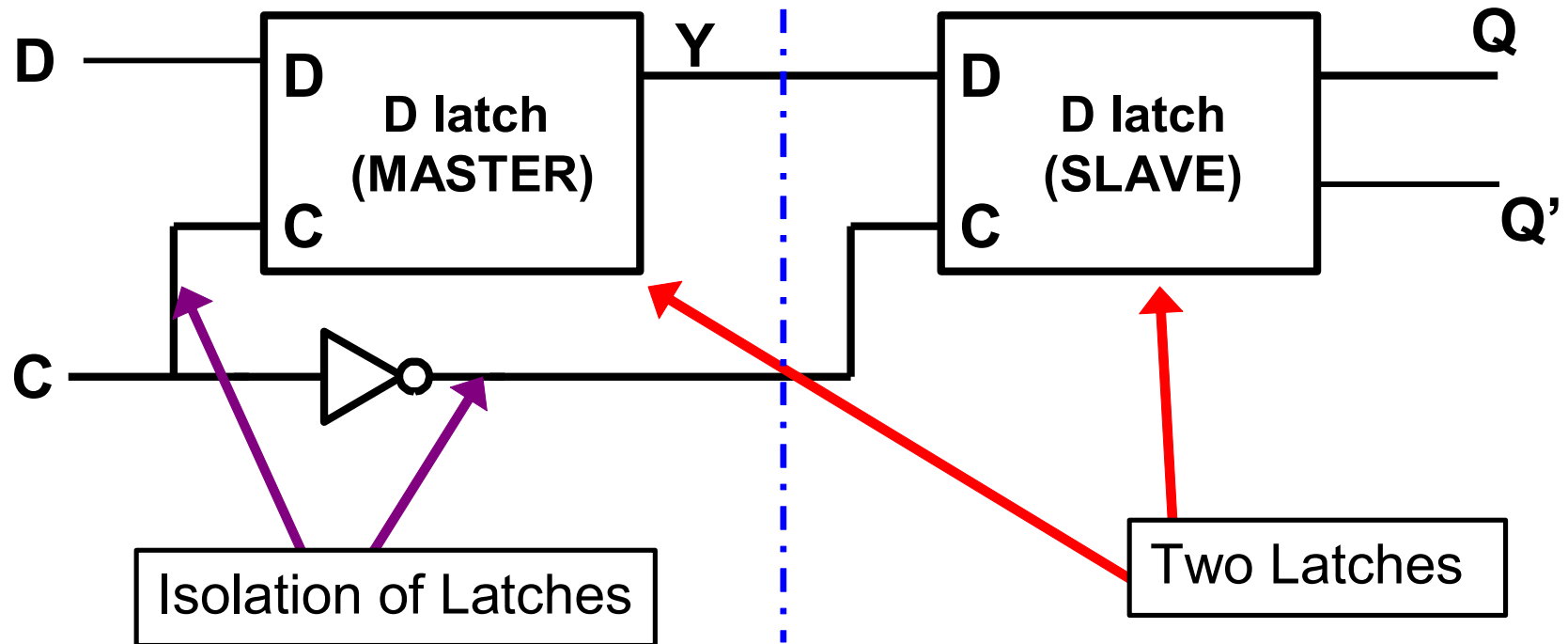


# D Type Master-Slave Flip-Flop (2/5)

 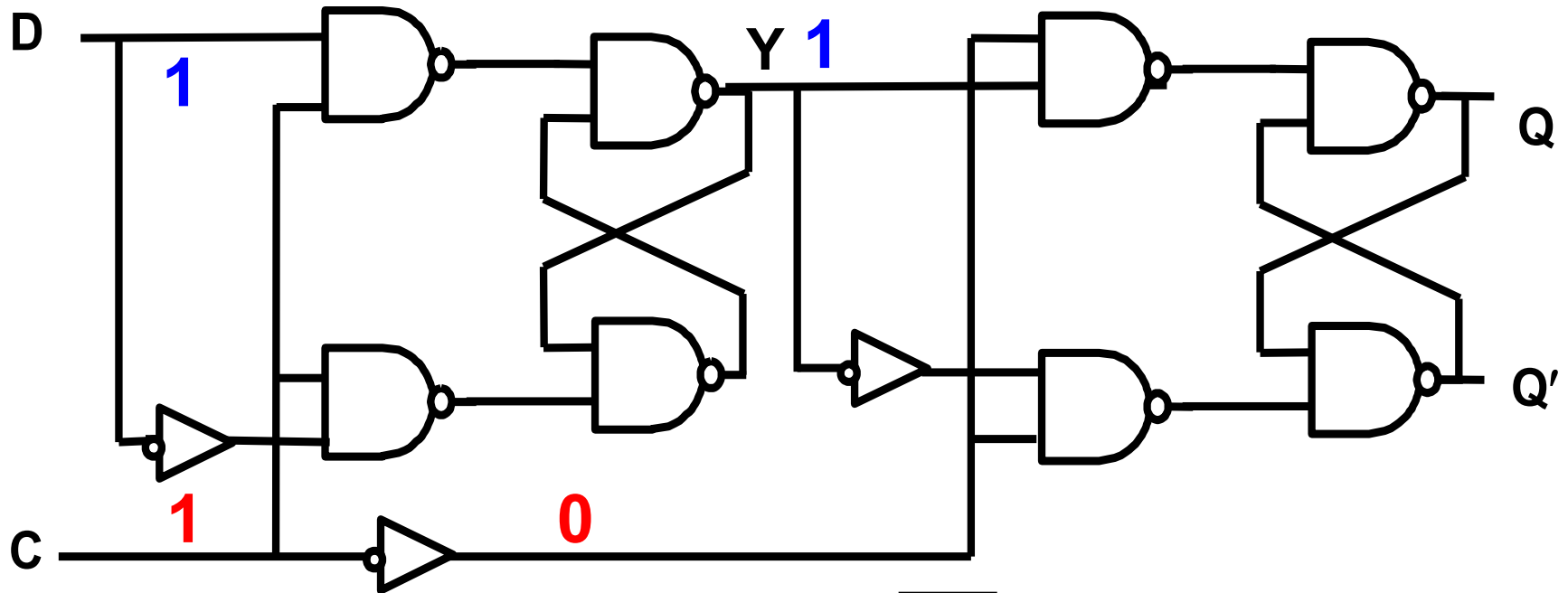

# D Type Master-Slave Flip-Flop (3/5)

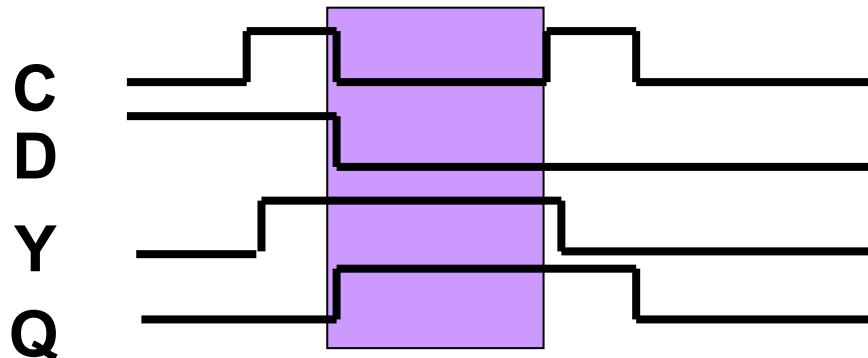 


# D Type Master-Slave Flip-Flop (4/5)

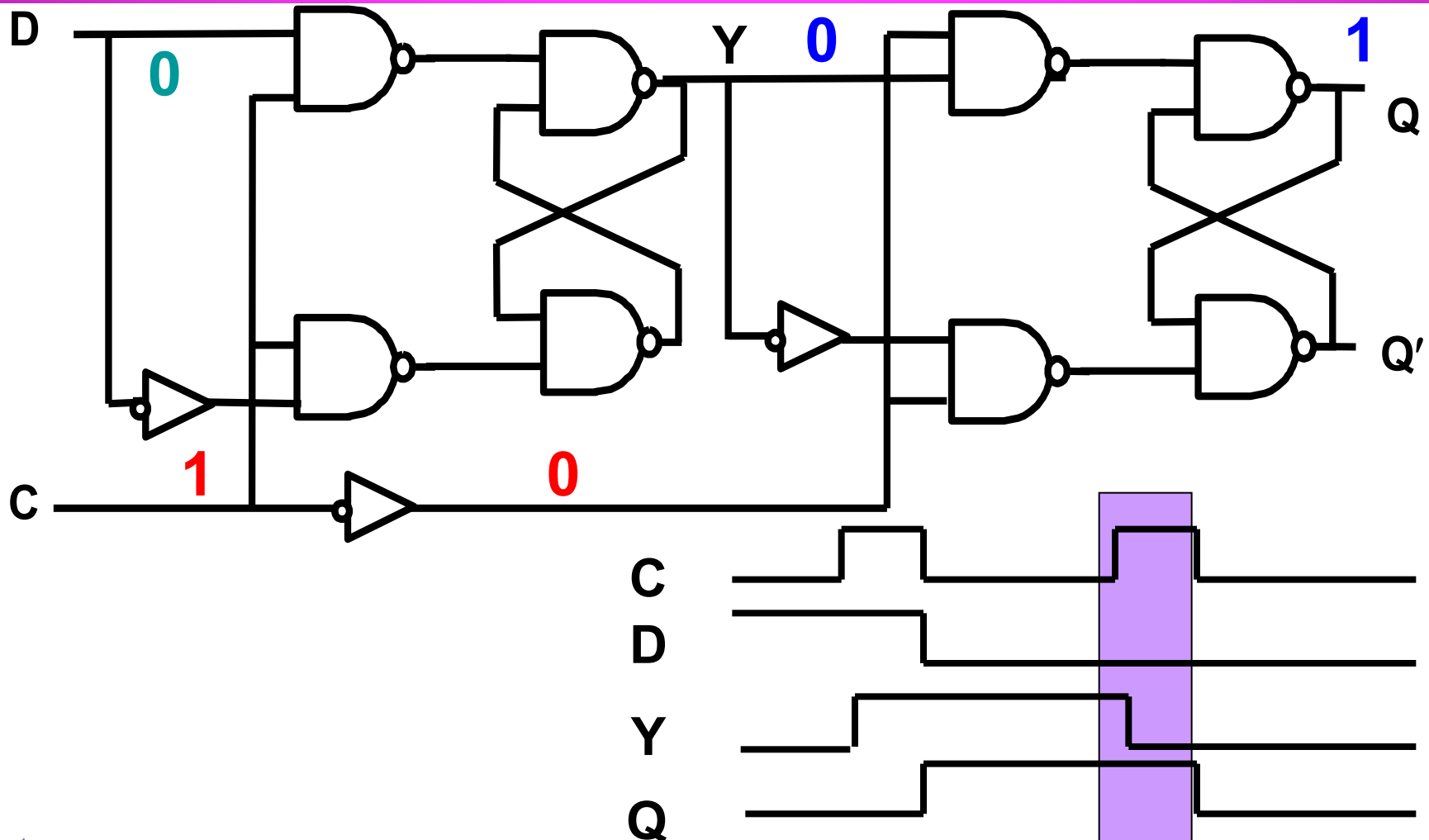




# D Type Master-Slave Flip-Flop (5/5)

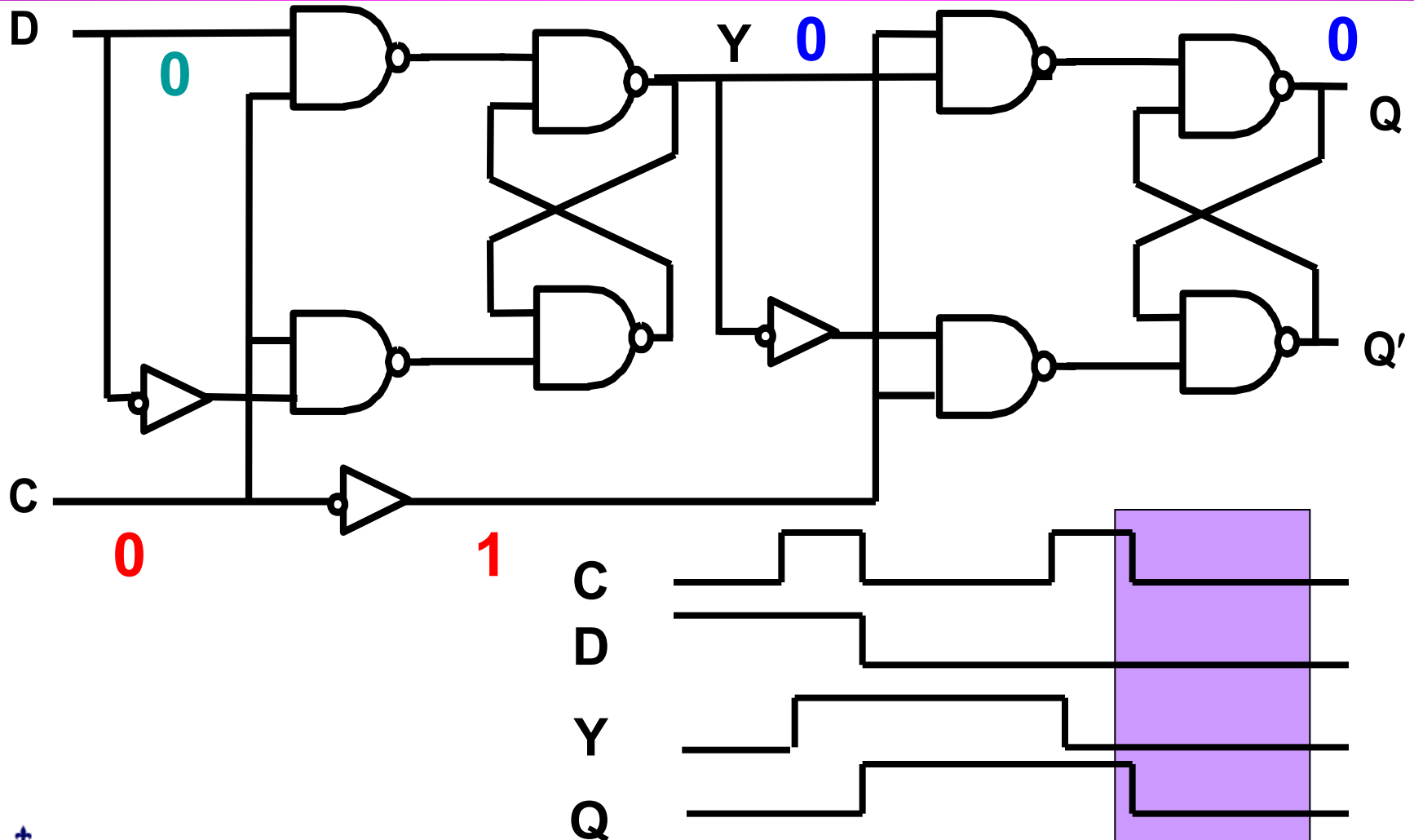
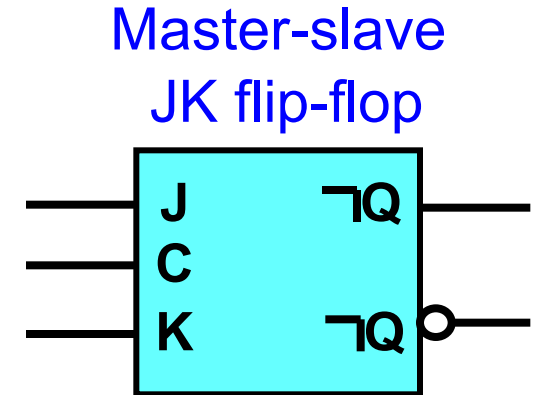
# JK Flip-Flops


- **JK Flip-Flop:**

- Uses 2 SR latches with control inputs.
  - The SR latch still has undesirable indeterminate next state (when **S** and **R** are both **1**).
- Adds **AND** gates to **S** and **R** inputs with feedback from the SR slave latch output.
  - Now when **S** and **R** inputs are **1**, the output of the flip-flop merely complements.
- Uses **narrow pulse clocking** approach.




Minimum pulse width for inputs, to avoid going into a metastable state.


# JK Type Master-Slave Flip-Flop

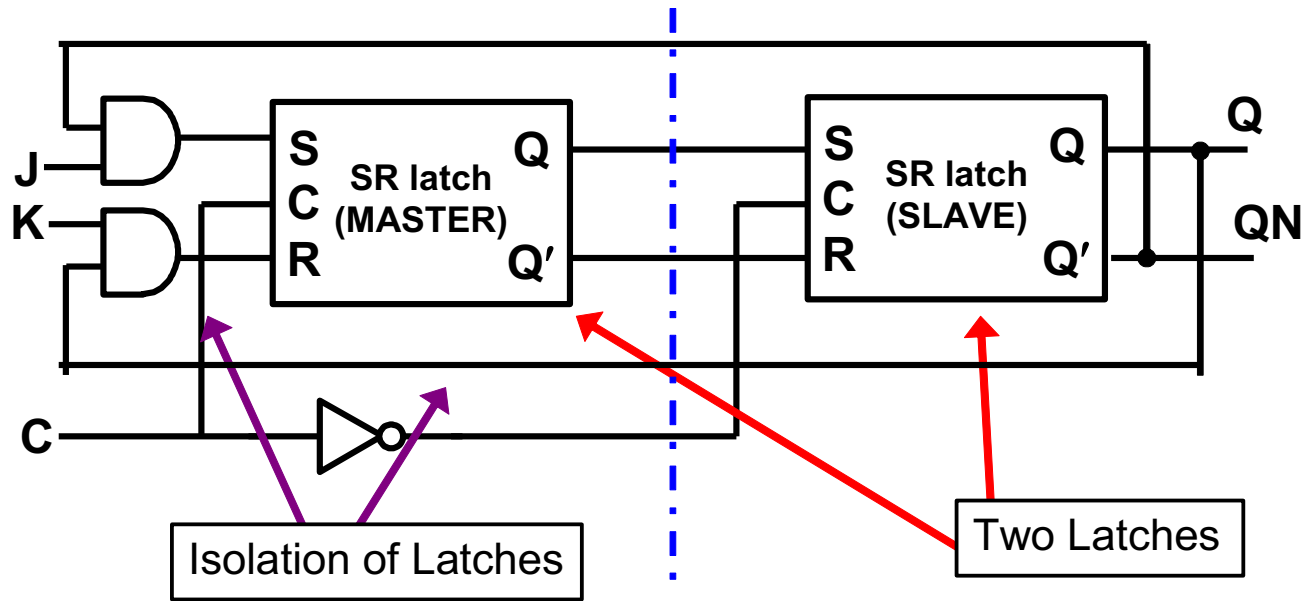

S	R	C	Q	QN
0	0	1	last Q	last QN
0	1	1	0	1
1	0	1	1	0
1	1	1	1	1
x	x	0	last Q	last QN

 

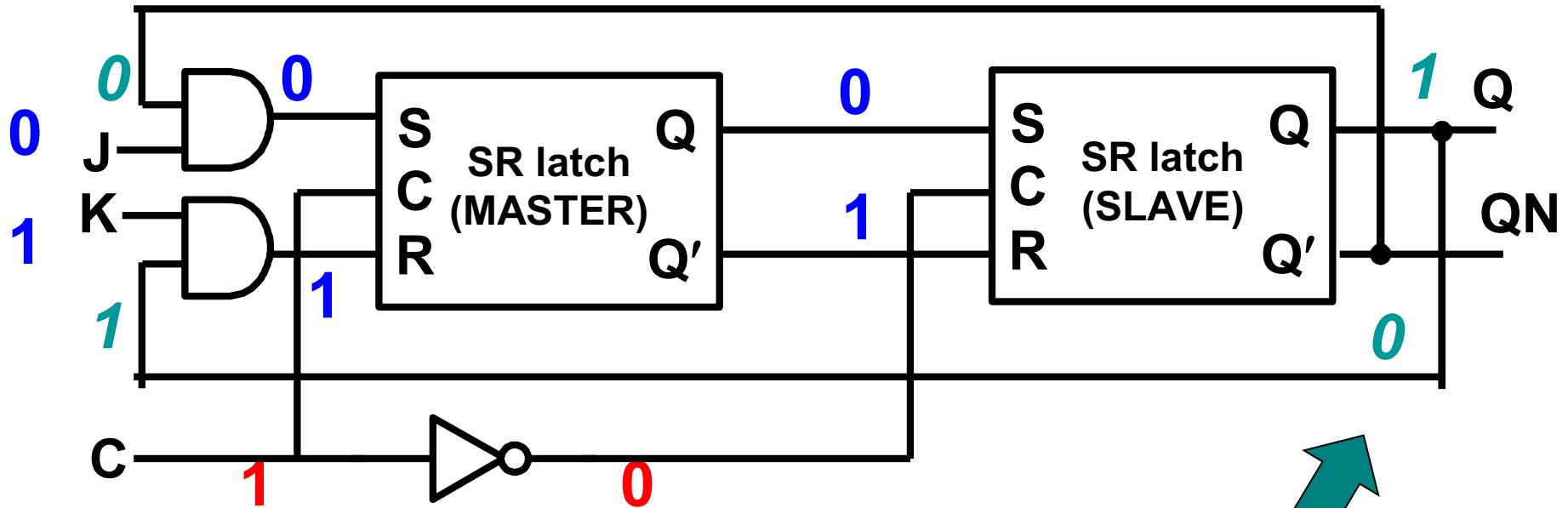
# Master-Slave JK Flip-Flop: $J=0, K=1$ (1/2)



S	R	C	Q	QN
0	0	1	last Q	last QN
0	1	1	0	1
1	0	1	1	0
1	1	1	1	1
x	x	0	last Q	last QN


Last Q & QN
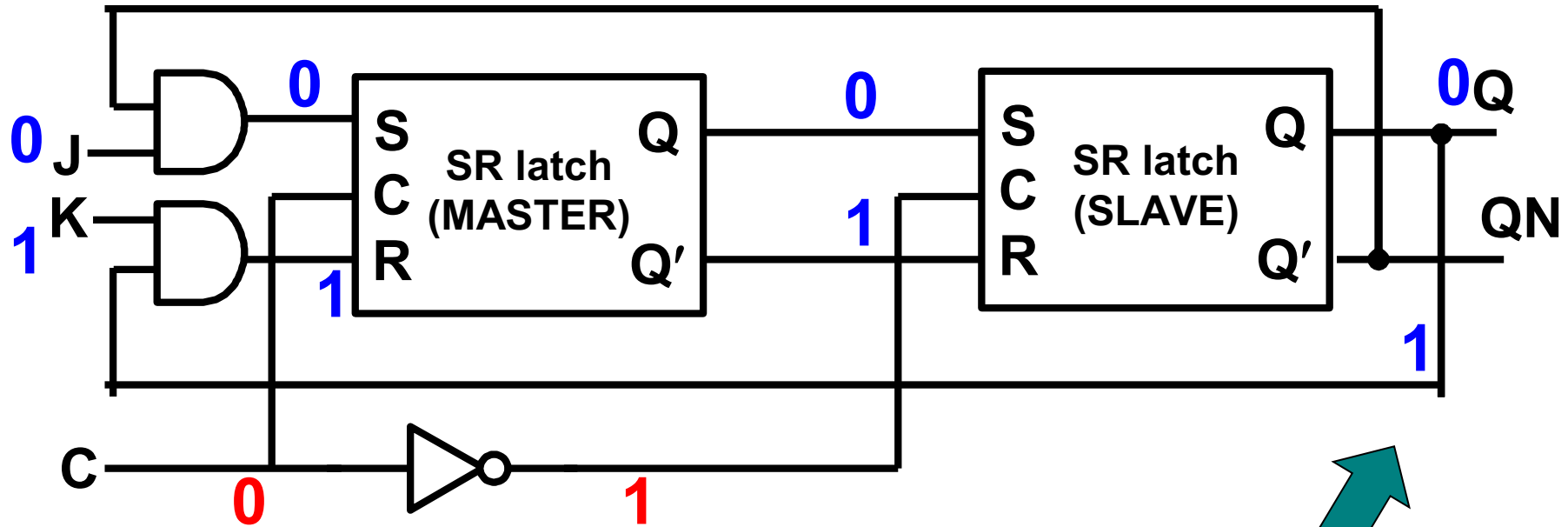
# Master-Slave JK Flip-Flop: $J=0, K=1$ (2/2)



S	R	C	Q	Q <sub>N</sub>
0	0	1	last Q	last Q <sub>N</sub>
0	1	1	0	1
1	0	1	1	0
1	1	1	1	1
x	x	0	last Q	last Q <sub>N</sub>

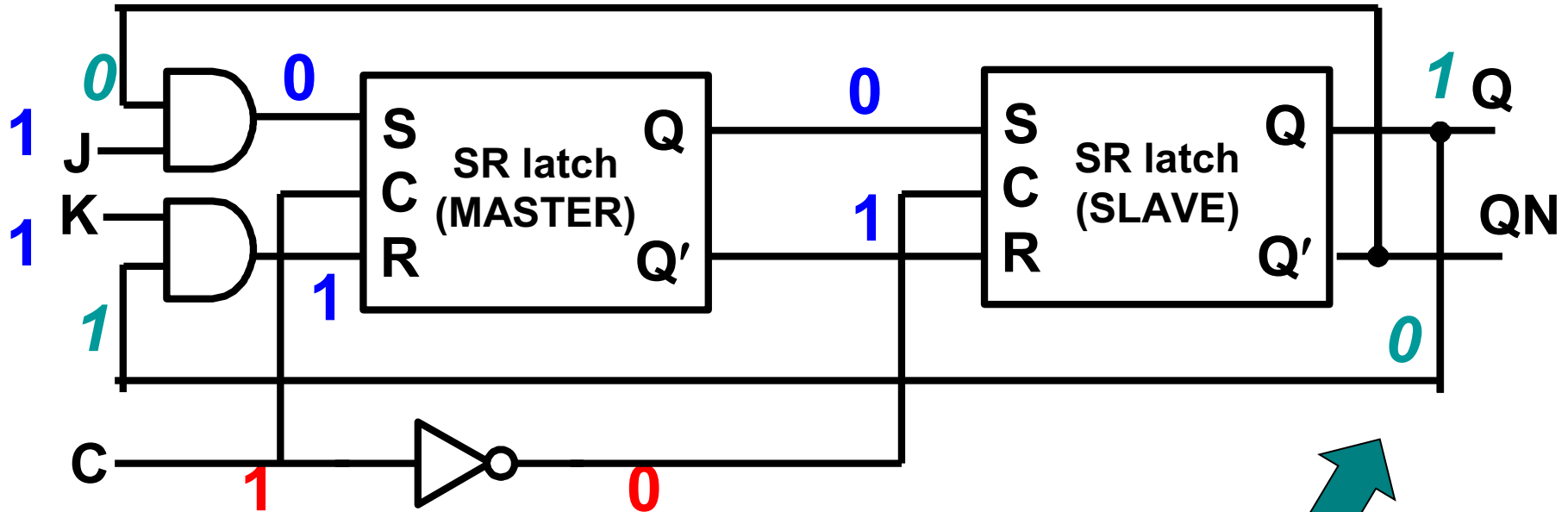
# Master-Slave JK Flip-Flop: $J=1, K=1$ (1/2)



S	R	C	Q	QN
0	0	1	last Q	last QN
0	1	1	0	1
1	0	1	1	0
1	1	1	1	1
x	x	0	last Q	last QN

Last Q & QN
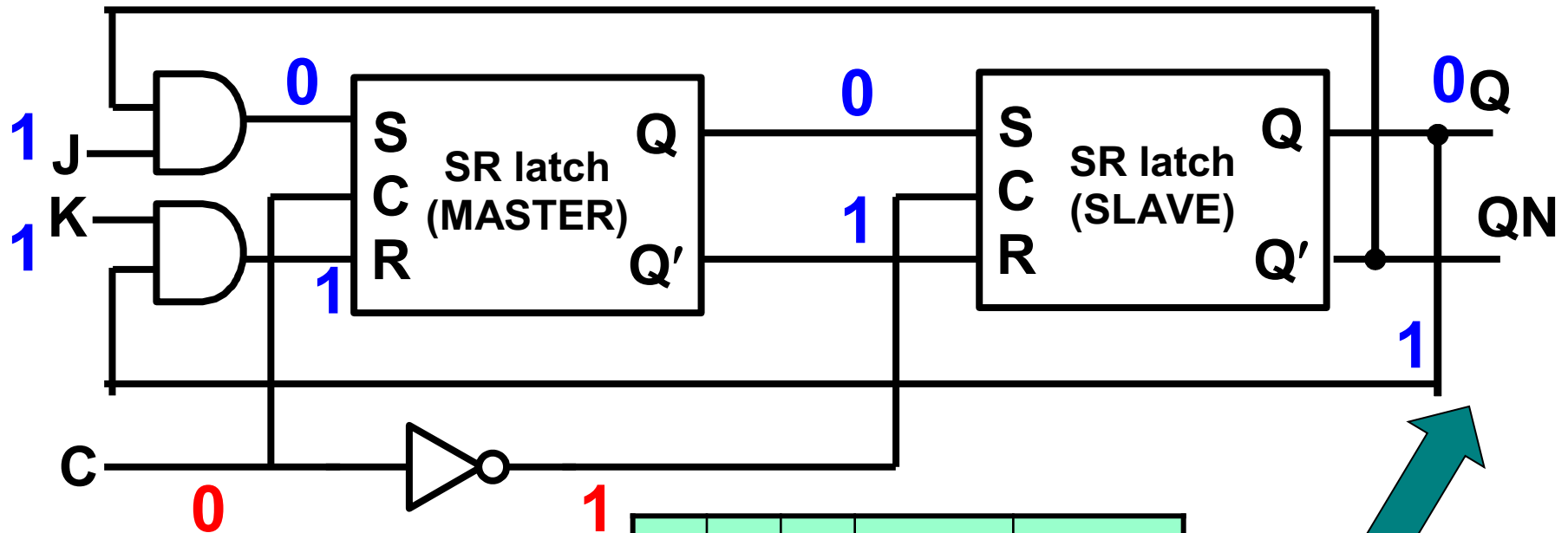
# Master-Slave JK Flip-Flop: $J=1, K=1$ (2/2)




S	R	C	Q	QN
0	0	1	last Q	last QN
0	1	1	0	1
1	0	1	1	0
1	1	1	1	1
x	x	0	last Q	last QN

J	K	C	Q	QN
x	x	0		
0	0	⌊		
0	1	⌊		
1	0	⌊		
1	1	⌊		

New Q & QN
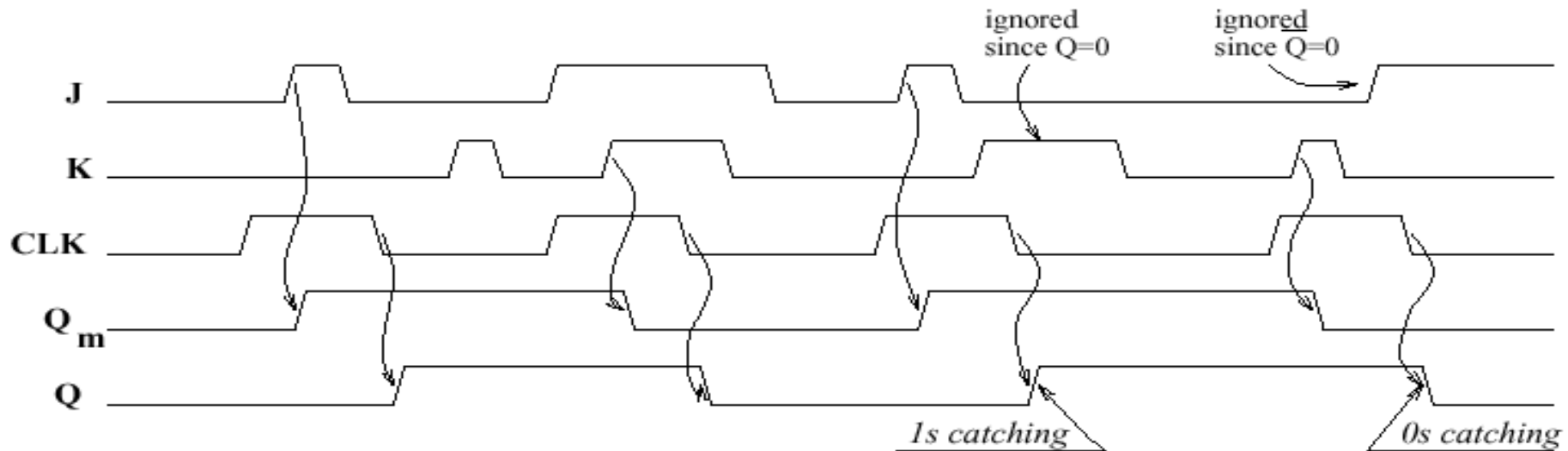
# Master-Slave JK Flip-Flop: Problems

- If inputs **J** and **K** are not held valid during the entire period when CLK is active for the master, the above flip-flop exhibits **1's and 0's catching behaviour**.
  - **1's Catching**: Output changes to **1** even though **K** and not **J** is asserted at the end of the triggering pulse.
  - **0's Catching**: Output changes to **0** even though **J** and not **K** is asserted at the end of the triggering pulse.






# Edge-Triggered Flip-Flops

- **Edge-triggered flip-flops:**



- **Ignore inputs** while the clock pulse is at a constant level.
- Only **set outputs** on clock pulse transitions.


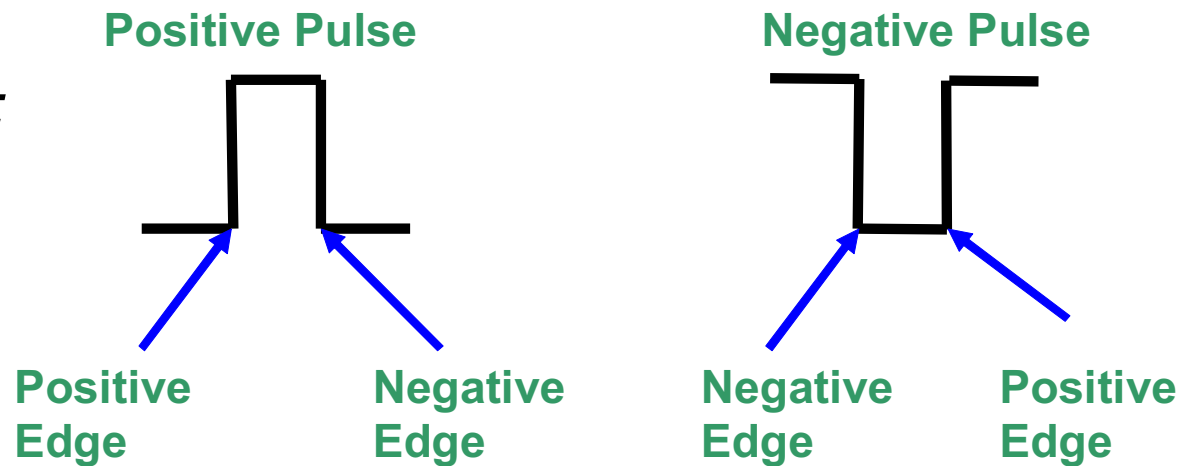
- *Negative or positive edges:*



- For **positive triggered flip-flops**, the value at the **D** input is transferred to **Q** on a positive transition.



# Positive Edge-Triggered D Flip-Flop

D	CLK	Q	QN
0		0	1
1		1	0
x	0	last Q	last QN
x	1	last Q	last QN

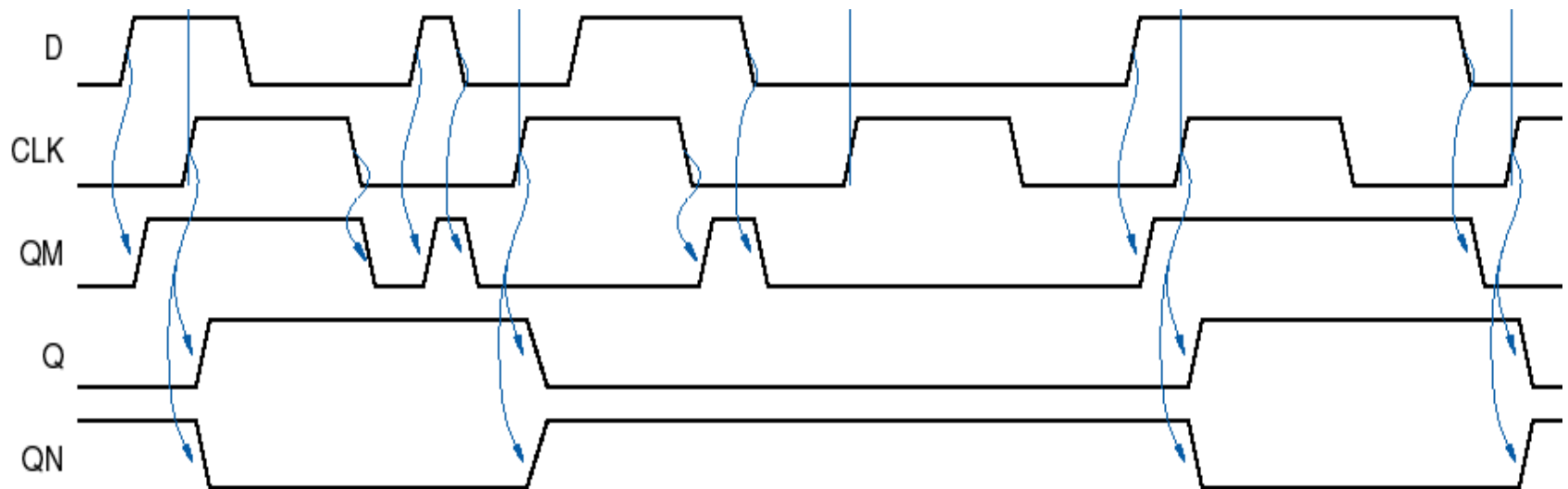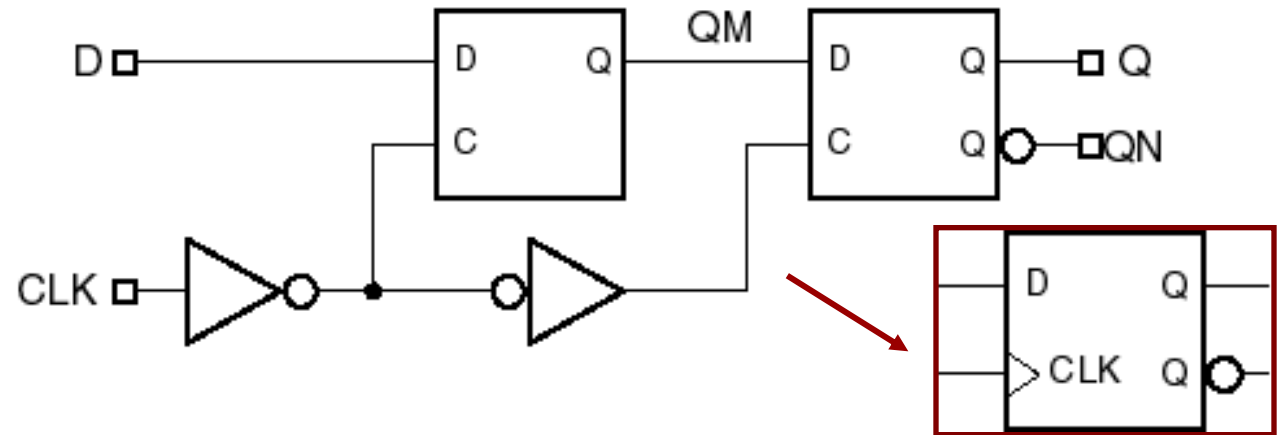

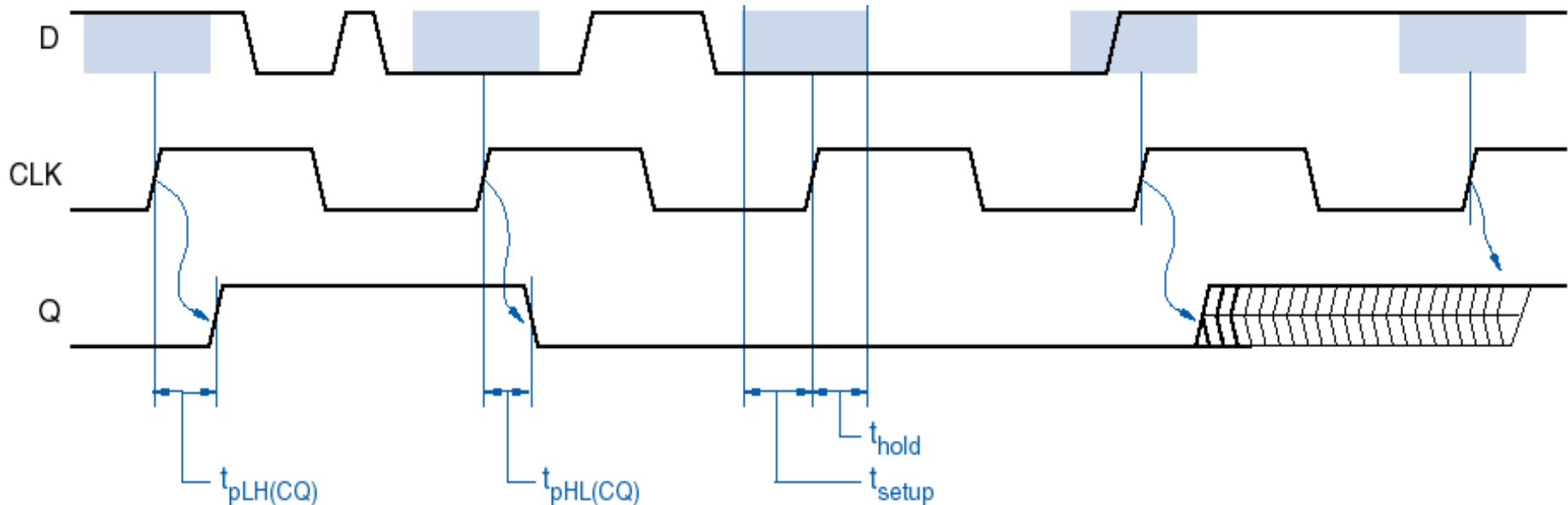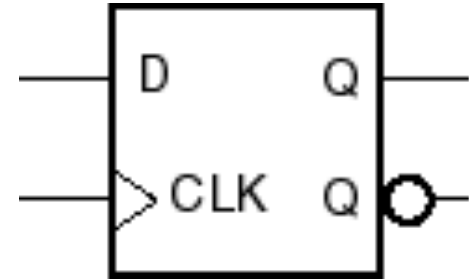 

# D Flip-Flop: Timing Parameters


- Timing parameters:
  - **Propagation delay** (from CLK).
  - **Setup time** ( $D$  before CLK).
  - **Hold time** ( $D$  after CLK).




# Other D Flip-Flop Variations

- **Negative-edge triggered:** By **inverting the clock input**, all the action takes place on the falling edge of CLK\_L (active low).
- It is the same as the first *master-slave flip-flop* we looked at!


D	CLK_L	Q	QN
0		0	1
1		1	0
x	0	last Q	last QN
x	1	last Q	last QN

 

# Edge Triggered JK Flip-Flop

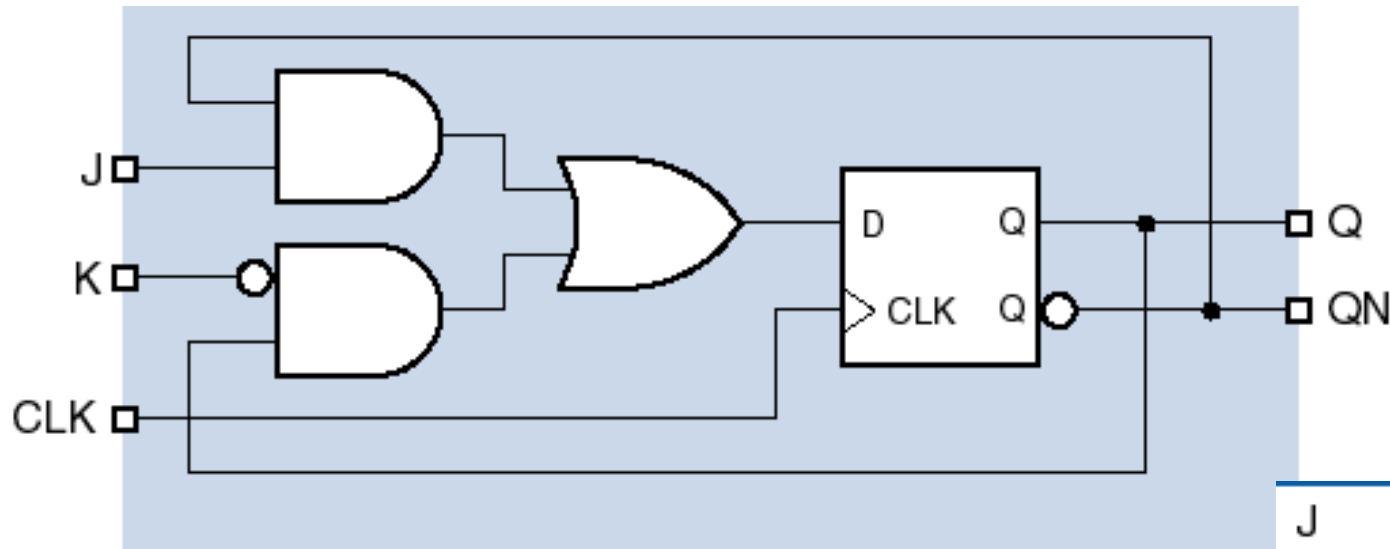


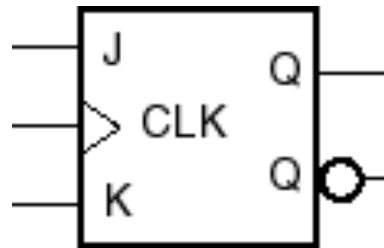**Solves the 1's and 0's catching problem of the master-slave!**



J	K	CLK	Q	QN
x	x	0	last Q	last QN
x	x	1	last Q	last QN
0	0		last Q	last QN
0	1		0	1
1	0		1	0
1	1		last QN	last Q


# Toggle flip-flop (T-Flip-Flop)

 


T	Q	Q'
0	0	0
0	1	1
1	0	1
1	1	0

- Using **T-Flip-Flops** the next state output is always *toggled*.
- The toggle flip-flop changes state when the input **T = 1**, and remains unchanged when **T = 0**.

# Toggle flip-flop (T-Flip-Flop)

 

D Flip-flop Conversion

 


JK Flip-flop Conversion

- The D-type flip-flop can be converted to a T flip-flop by **connecting the Q' output directly to the D-input** with the toggling signal **T being the clock input**. So, when the D flip-flop is triggered by the clock ( $T=1$ ), the next Q output will be the **compliment of the current Q**.
- The JK flip-flop can be converted to a toggle flip-flop by **connecting both the J and K inputs together**. So, when both J and K are 0 ( $T=0$ ), we have **last Q** as the output and when both J and K are 1, the output **changes state**.
 
# Applications of Flip-Flops (1/2)

- **Parallel Data Storage:**

- In digital systems, data is normally stored in groups of bits to represent e.g., numbers or codes.
- We can take several bits of data on parallel lines and store them simultaneously in a group of flip-flops (**Register**).





 
# Applications of Flip-Flops (2/2)

- **Digital Counters:**

- The 2-bit binary sequence is repeated every 4 clock pulses.
- When it reaches the value 3, it resets back to 0 and the sequence begins again.



You can use **Toggle Flip-Flop** instead

# Task 2

- Determine the output states for the flip-flop below, given the pulse inputs shown.

